

# Large Signal and Resistive Biasing of BJT

Lab 5 — ECEN 222: Electronic Circuits

University of Nebraska–Lincoln  
Department of Electrical and Computer Engineering

---

## 1 Objectives

The primary objective of this lab is to investigate the fundamental principles of DC biasing for bipolar junction transistors (BJTs) and analyze large-signal behavior in common biasing configurations. Building upon the I-V characteristics studied in Lab 2, this lab focuses on establishing and maintaining stable DC operating points (Q-points) that are essential for proper amplifier operation. Upon completion of this lab, students will be able to design and analyze fixed-bias circuits, understand the limitations of fixed-bias configurations and the effects of  $\beta$  variations, design and implement voltage-divider bias circuits, analyze the four-resistor bias network and understand its stability characteristics and experimentally determine DC operating points. Through hands-on measurements and analysis, students will design robust bias circuits, preparing them for subsequent labs on small-signal amplifiers and frequency response.

## 2 Pre-Lab Preparation

Before arriving at the lab session, students are required to thoroughly prepare by reading the relevant material from the course textbook. Specifically, read Chapter 5 (Bipolar Junction Transistors) in Sedra & Smith, with particular emphasis on sections covering DC biasing arrangements, the four-resistor bias network, bias stability, and graphical analysis using load lines. Review the concept of the Q-point (quiescent operating point) and understand why proper biasing is critical for linear amplification. Additionally, review Thévenin equivalent circuit analysis, as this technique is essential for analyzing voltage-divider bias circuits. Ensure you understand Kirchhoff's voltage and current laws and are comfortable with iterative circuit analysis techniques. Students must also complete the pre-lab questions provided in Section 5 and come prepared with calculated component values for the circuits to be built. Bring engineering graph paper or be prepared to create load-line plots from your data. Proper preparation will ensure efficient use of lab time and deeper understanding of the practical challenges of BJT biasing.

## 3 Background Theory

### 3.1 The Need for Biasing

In Lab 4, we explored the fundamental I-V characteristics of BJTs and observed their operation in cutoff, active, and saturation regions. For a BJT to function as a linear amplifier, it must be biased to operate in the active region with a stable DC operating point, also called the quiescent point or Q-point. The Q-point defines the DC collector current ( $I_C$ ), base current ( $I_B$ ), and collector-emitter voltage ( $V_{CE}$ ) when no AC signal is applied.

Proper biasing serves several critical purposes:

- **Ensures active-region operation:** The bias must keep the base-emitter junction forward-biased and the base-collector junction reverse-biased.

- **Provides maximum output voltage swing:** The Q-point should be positioned to allow the AC signal to swing symmetrically without driving the transistor into cutoff or saturation.
- **Maintains stability:** The bias circuit should maintain a relatively constant Q-point despite variations in transistor parameters ( $\beta$ ,  $V_{BE}$ ) due to manufacturing tolerances and temperature changes.
- **Establishes proper small-signal parameters:** The DC operating point determines the small-signal parameters (transconductance  $g_m$ , input resistance  $r_\pi$ ) that govern AC amplification.

Without proper biasing, the transistor may operate non-linearly, causing signal distortion, or may drift between operating regions due to temperature changes, making the circuit unreliable.

### 3.2 DC Load Line Analysis

A powerful graphical technique for analyzing BJT bias circuits is the DC load line. The load line represents all possible combinations of  $V_{CE}$  and  $I_C$  that satisfy Kirchhoff's voltage law around the collector-emitter circuit loop.

Consider a generic common-emitter circuit with a resistor  $R_C$  in series with the collector and supply voltage  $V_{CC}$ , and a resistor  $R_E$  in series with the emitter. Applying KVL around the collector-emitter loop:

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E \quad (1)$$

Since  $I_E \approx I_C$  (because  $I_E = I_C + I_B$  and  $I_B \ll I_C$  for typical  $\beta$  values), we can write:

$$V_{CC} = I_C (R_C + R_E) + V_{CE} \quad (2)$$

Rearranging to express  $I_C$  as a function of  $V_{CE}$ :

$$I_C = \frac{V_{CC} - V_{CE}}{R_C + R_E} \quad (3)$$

This is a linear equation with two convenient endpoints:

- When  $V_{CE} = 0$  (saturation):  $I_C = I_{C,sat} = \frac{V_{CC}}{R_C + R_E}$
- When  $I_C = 0$  (cutoff):  $V_{CE} = V_{CE,cutoff} = V_{CC}$

The DC load line is plotted on the output characteristic curves ( $I_C$  vs.  $V_{CE}$ ) from Lab 2. The intersection of the load line with a particular  $I_B$  curve determines the Q-point for that base current. The load line slope is  $-1/(R_C + R_E)$ .

The Q-point must satisfy both the transistor characteristics (the  $I_B$  curves) and the external circuit constraints (the load line). For a given base bias current  $I_B$ , the Q-point is uniquely determined by the intersection of the corresponding  $I_B$  curve with the load line.

### 3.3 Bias Stability and Temperature Effects

BJT parameters vary significantly with temperature:

- $V_{BE}$  decreases by approximately 2 mV/°C
- $\beta$  typically increases with temperature
- Reverse saturation current  $I_{CO}$  approximately doubles every 10°C

A well-designed bias circuit must maintain a stable Q-point despite these variations. The voltage-divider bias with adequate emitter degeneration ( $R_E$ ) provides the best stability because:

1. The base voltage  $V_B$  is fixed by the stiff divider, independent of transistor parameters
2. The emitter resistor provides strong negative feedback
3. Changes in  $V_{BE}$  have minimal effect since  $V_E = V_B - V_{BE}$  and  $V_B \gg V_{BE}$  typically

## 4 Experimental Procedures

### 4.1 Part 1: Fixed-Bias Circuit Analysis

#### 4.1.1 Fixed-Bias Configuration Theory

The simplest biasing arrangement is the fixed-bias or base-bias circuit shown in Figure 1. A single resistor  $R_B$  connects the base to the positive supply  $V_{CC}$ , providing base current.

 


Figure 1: Fixed-bias (base-bias) configuration.

Analyzing the base circuit by KVL:

$$V_{CC} = I_B R_B + V_{BE} \quad (4)$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} \quad (5)$$

The collector current is then:

$$I_C = \beta I_B = \beta \frac{V_{CC} - V_{BE}}{R_B} \quad (6)$$

And the collector-emitter voltage from the collector loop KVL:

$$V_{CE} = V_{CC} - I_C R_C \quad (7)$$

#### Limitations of Fixed Bias:

The fixed-bias configuration has a critical weakness: the Q-point is highly dependent on  $\beta$ . Since  $\beta$  varies significantly between transistors of the same type (typically  $\pm 50\%$  or more) and also changes with temperature and collector current, the fixed-bias circuit produces an unstable Q-point.

Consider two transistors with  $\beta_1 = 100$  and  $\beta_2 = 200$ . From Equation 6, the collector current for the second transistor would be twice that of the first, drastically shifting the Q-point. This makes fixed bias impractical for mass production and for applications where temperature varies.

A stability factor  $S$  can be defined to quantify bias stability:

$$S = \left. \frac{\partial I_C}{\partial I_{CO}} \right|_{I_B = \text{const}} \quad (8)$$

where  $I_{CO}$  is the collector reverse saturation current, which doubles approximately every  $10^\circ\text{C}$ . For fixed bias,  $S$  approaches  $\beta + 1$ , indicating very poor stability.

#### 4.1.2 Fixed-Bias Circuit Experiment

In this section, you will construct and analyze a fixed-bias circuit to understand its operation and limitations, particularly its sensitivity to  $\beta$  variations.

**Design Calculations:**

Design a fixed-bias circuit (Figure 1) with the following specifications:

- $V_{CC} = 12\text{ V}$
- Desired  $I_C = 2\text{ mA}$
- Desired  $V_{CE} = 6\text{ V}$  (centered Q-point)
- Assume  $\beta = 120$  and  $V_{BE} = 0.7\text{ V}$

Calculate:

1. Required  $R_C$  from Equation 7:

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} \quad (9)$$

2. Required  $I_B$  from  $I_C = \beta I_B$ :

$$I_B = \frac{I_C}{\beta} \quad (10)$$

3. Required  $R_B$  from Equation ??:

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} \quad (11)$$

Select standard resistor values closest to your calculated values.

**Construction and Measurement:**

Construct the circuit on your breadboard using the calculated component values. Measure and record:

1. DC voltages:  $V_B$ ,  $V_C$ ,  $V_E$
2. Calculate  $V_{BE}$  and  $V_{CE}$
3. Calculate currents:  $I_B$  and  $I_C$
4. Calculate actual  $\beta$

Compare your measured Q-point with the designed values. Explain any discrepancies.

 **$\beta$  Sensitivity Test:**

Test the circuit in Figure 1 and find:

- Measure the Q-point ( $I_C$ ,  $V_{CE}$ )
- Calculate the actual  $\beta$

Calculate the change in  $I_C$ . This demonstrates the poor stability of fixed bias.

In your lab report, summarize the results and discuss the implications for circuit design. Calculate the sensitivity  $\partial I_C / \partial \beta$  and compare with theoretical predictions.

**4.2 Part 2: Load-Line Analysis of Fixed-Bias Circuit**

Using the fixed-bias circuit from Part 1, you will now perform a graphical load-line analysis.

**Theoretical Load Line:**

For the fixed-bias circuit with no emitter resistor, the load line equation from Equation 3 simplifies to:

$$I_C = \frac{V_{CC} - V_{CE}}{R_C} \quad (12)$$

Calculate the two endpoints:

- $I_{C,sat} = V_{CC} / R_C$  (when  $V_{CE} = 0$ )

- $V_{CE,cutoff} = V_{CC}$  (when  $I_C = 0$ )

Plot the DC load line using these two points on axes of  $I_C$  (vertical, 0 to  $I_{C,sat}$ ) versus  $V_{CE}$  (horizontal, 0 to  $V_{CC}$ ).

### Experimental Output Characteristics:

You will now measure several points on the output characteristics for different base currents, similar to Lab 4 but focused on the specific region near your Q-point.

Select three base current values:  $I_B = 10 \mu\text{A}$ ,  $20 \mu\text{A}$ , and  $30 \mu\text{A}$ . For each fixed  $I_B$ :

1. Adjust  $R_B$  to achieve the desired base current (measure voltage across  $R_B$  to verify)
2. Vary  $V_{CC}$  from 0 V to 12 V
3. For each  $V_{CC}$ , measure  $V_{CE}$  and  $I_C$
4. Plot the three curves on the same graph as your load line

Mark your actual Q-point (from Part 1 measurements) on the graph. It should lie at the intersection of the load line and the curve corresponding to your measured  $I_B$ .

Verify that the graphical Q-point matches your measured Q-point. Discuss any discrepancies and potential sources of error.

## 4.3 Part 3: Emitter-Bias Circuit

### 4.3.1 Emitter-Bias Configuration Theory

An improvement over fixed bias is the emitter-bias configuration, which adds an emitter resistor  $R_E$  as shown in Figure 2.

 


Figure 2: Emitter-bias configuration with emitter degeneration resistor.

The emitter resistor provides negative feedback that stabilizes the Q-point. Analyzing the base-emitter loop:

$$V_{CC} = I_B R_B + V_{BE} + I_E R_E \quad (13)$$

Since  $I_E = (\beta + 1)I_B$ :

$$V_{CC} = I_B R_B + V_{BE} + (\beta + 1)I_B R_E \quad (14)$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E} \quad (15)$$

The collector current is:

$$I_C = \beta I_B = \frac{\beta(V_{CC} - V_{BE})}{R_B + (\beta + 1)R_E} \quad (16)$$

If  $(\beta + 1)R_E \gg R_B$ , then:

$$I_C \approx \frac{\beta(V_{CC} - V_{BE})}{(\beta + 1)R_E} \approx \frac{V_{CC} - V_{BE}}{R_E} \quad (17)$$

This approximation shows that  $I_C$  becomes nearly independent of  $\beta$ , providing much better stability. The emitter resistor creates a self-regulating mechanism: if  $I_C$  tries to increase, the voltage drop across  $R_E$  increases, which reduces  $V_{BE}$ , which in turn reduces  $I_C$ , counteracting the original increase.

### 4.3.2 Emitter-Bias Circuit Experiment

Now construct an emitter-bias circuit (Figure 2) to observe the improved stability provided by emitter degeneration.

#### Design Calculations:

Design for the same Q-point as Part 1:

- $V_{CC} = 12$  V
- Desired  $I_C = 2$  mA
- Desired  $V_{CE} = 6$  V
- Choose  $V_E = 2$  V (providing some stability margin)
- Assume  $\beta = 120$  and  $V_{BE} = 0.7$  V

Calculate:

1. Emitter resistor  $R_E$
2. Collector resistor  $R_C$
3. Base voltage  $V_B$
4. Base current  $I_B$
5. Base resistor  $R_B$

#### Construction and Measurement:

Construct the circuit and measure:

- $V_B, V_C, V_E$
- Calculate  $V_{BE}$  and  $V_{CE}$
- Calculate  $I_B, I_C, I_E$
- Calculate actual  $\beta$

## 4.4 Part 4: Voltage-Divider Bias Design and Analysis

### 4.4.1 Voltage-Divider Bias Configuration Theory

The most widely used and stable biasing configuration is the voltage-divider bias or four-resistor bias network shown in Figure 3.

This configuration uses a voltage divider ( $R_1$  and  $R_2$ ) to establish a fixed base voltage, combined with an emitter resistor  $R_E$  to stabilize the emitter current.

The base voltage is determined by the voltage divider (assuming the base current is small enough not to significantly load the divider):

 


Figure 3: Voltage-divider bias (four-resistor bias network).

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} \quad (18)$$

The emitter voltage is:

$$V_E = V_B - V_{BE} \quad (19)$$

The emitter current is:

$$I_E = \frac{V_E}{R_E} = \frac{V_B - V_{BE}}{R_E} \quad (20)$$

Since  $I_C \approx I_E$ :

$$I_C \approx \frac{V_B - V_{BE}}{R_E} \quad (21)$$

The collector-emitter voltage is found from the collector loop:

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E \approx V_{CC} - I_C (R_C + R_E) \quad (22)$$

### Thévenin Equivalent Analysis:

For more accurate analysis, especially when the base current is not negligible, we can replace the base bias network with its Thévenin equivalent:

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2} \quad (23)$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2 \quad (24)$$

Applying KVL to the base-emitter loop with the Thévenin equivalent:

$$V_{TH} = I_B R_{TH} + V_{BE} + I_E R_E \quad (25)$$

$$V_{TH} = I_B R_{TH} + V_{BE} + (\beta + 1) I_B R_E \quad (26)$$

Solving for  $I_B$ :

$$I_B = \frac{V_{TH} - V_{BE}}{R_{TH} + (\beta + 1) R_E} \quad (27)$$

And therefore:

$$I_C = \beta I_B = \frac{\beta(V_{TH} - V_{BE})}{R_{TH} + (\beta + 1)R_E} \quad (28)$$

### Design Guidelines for Voltage-Divider Bias:

For good stability, the following design guidelines are recommended:

1. **Stiff voltage divider:** Choose  $R_1$  and  $R_2$  such that the current through the divider is much larger than the base current (typically 10 times larger). This ensures that  $V_B$  remains relatively constant despite variations in  $I_B$ .
2. **Adequate emitter voltage:** Set  $V_E \approx V_{CC}/10$  to  $V_{CC}/5$  to provide good stabilization. A common choice is  $V_E = 0.1V_{CC}$  to  $0.2V_{CC}$ .
3. **Centered Q-point:** For maximum output swing, position the Q-point near the middle of the load line by choosing  $V_{CE} \approx V_{CC}/2$ .
4. **Ensure active-region operation:** Verify that  $V_{CE} > V_{CE,sat} \approx 0.3$  V and  $V_{CE} > V_E$  (which ensures the collector-base junction is reverse-biased).

The stability factor for voltage-divider bias can be approximated as:

$$S \approx \frac{(\beta + 1)(R_{TH} + R_E)}{R_{TH} + (\beta + 1)R_E} \quad (29)$$

For a stiff divider where  $R_{TH} \ll (\beta + 1)R_E$ , this approaches  $S \approx 1$ , indicating excellent stability.

#### 4.4.2 Voltage-Divider Bias Circuit Experiment

In this section, you will design, construct, and thoroughly analyze a voltage-divider bias circuit—the industry-standard biasing configuration.

### Design Calculations:

Design a voltage-divider bias circuit (Figure 3) with specifications:

- $V_{CC} = 12$  V
- Desired  $I_C = 2$  mA
- Desired  $V_{CE} = 6$  V (centered Q-point for maximum swing)
- Choose  $V_E = 2$  V (approximately  $V_{CC}/6$ )
- Assume  $\beta = 120$  and  $V_{BE} = 0.7$  V

Follow this systematic design procedure:

1. Calculate emitter resistor  $R_E$
2. Calculate collector resistor  $R_C$
3. Calculate base voltage  $V_B$
4. Choose divider current (approximately 10 times  $I_B$ )
5. Calculate  $R_2$
6. Calculate  $R_1$

Verify your design using Thévenin equivalent analysis:

$$V_{TH} = V_{CC} \frac{R_2}{R_1 + R_2} \quad (30)$$



$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} \quad (31)$$

Then calculate  $I_B$  from Equation 27 and verify that  $I_C = \beta I_B \approx 2 \text{ mA}$ .

### Construction and Measurement:

Construct the circuit using standard resistor values. Measure:

1. All node voltages:  $V_B$ ,  $V_C$ ,  $V_E$  (with respect to ground)
2. Voltage across each resistor:
  - $V_{R_1}$  (to calculate current through voltage divider)
  - $V_{R_2}$
  - $V_{R_C}$  (to calculate  $I_C$ )
  - $V_{R_E}$  (to calculate  $I_E$ )
3. Calculate all voltages of interest:
  - $V_{BE} = V_B - V_E$
  - $V_{CE} = V_C - V_E$
  - $V_{CB} = V_C - V_B$  (should be negative for active region)
4. Calculate all currents:
  - $I_C = V_{R_C}/R_C = (V_{CC} - V_C)/R_C$
  - $I_E = V_{R_E}/R_E = V_E/R_E$
  - $I_B = I_E - I_C$  (from KCL)
  - Divider current:  $I_1 = (V_{CC} - V_B)/R_1$
5. Calculate  $\beta = I_C/I_B$
6. Verify that  $I_1 \gg I_B$  (stiff divider condition)

Create a comprehensive table in your report with designed values, measured values, and percentage errors.

### Verify Active-Region Operation:

Check that all conditions for active mode are satisfied:

- $V_{BE} \approx 0.6$  to  $0.7 \text{ V}$  (forward-biased)
- $V_{CB} < 0$  or equivalently  $V_C > V_B$  (reverse-biased collector-base junction)
- $V_{CE} > V_{CE,sat} \approx 0.3 \text{ V}$

### Load-Line Analysis:

Calculate and plot the DC load line for this circuit. The saturation current is:

$$I_{C,sat} = \frac{V_{CC}}{R_C + R_E} \quad (32)$$

Plot the load line and mark your measured Q-point. The Q-point should lie near the center of the load line if your design is correct.

## 5 Pre-Lab Questions

Complete these questions before coming to the lab session. Include your answers and all supporting work in your lab report.

1. For a fixed-bias circuit with  $V_{CC} = 12\text{ V}$ ,  $R_B = 470\text{ k}\Omega$ ,  $R_C = 2.2\text{ k}\Omega$ ,  $\beta = 150$ , and  $V_{BE} = 0.7\text{ V}$ :
  - (a) Calculate  $I_B$ ,  $I_C$ , and  $V_{CE}$
  - (b) Verify that the transistor is in the active region
  - (c) If  $\beta$  changes to 100, recalculate  $I_C$  and  $V_{CE}$
  - (d) Calculate the percentage change in  $I_C$  due to the  $\beta$  variation
  - (e) Calculate the saturation current  $I_{C,sat}$  and cutoff voltage  $V_{CE,cutoff}$  for the load line

Show all calculations clearly.

2. Design a voltage-divider bias circuit to meet the following specifications:

- $V_{CC} = 15\text{ V}$
- $I_C = 3\text{ mA}$
- $V_{CE} = 7.5\text{ V}$  (centered Q-point)
- $V_E = 2.5\text{ V}$
- $\beta = 100$  (nominal)
- Stiff divider with  $I_{R_1} = 10I_B$

Calculate all four resistor values ( $R_1$ ,  $R_2$ ,  $R_C$ ,  $R_E$ ). Verify your design by calculating the actual Q-point with your selected standard values.

3. For the DC load line:
  - (a) Derive the load-line equation for a common-emitter circuit with both  $R_C$  and  $R_E$  present
  - (b) Explain how the slope of the load line changes when  $R_E$  is added

## 6 Additional Analysis (For Lab Report)

In your lab report, include the following additional analysis and discussion:

1. **Comparison Table:** Create a comprehensive comparison table summarizing the three bias configurations tested (fixed bias, emitter bias, voltage-divider bias). Include columns for:
  - Number of components
  - Designed Q-point
  - Measured Q-point
  - Advantages and disadvantages
  - Typical applications
2. **Design Optimization:** Discuss the design trade-offs in voltage-divider bias:
  - Stiffer divider (smaller  $R_1$ ,  $R_2$ ) improves stability but increases quiescent power consumption
  - Larger  $R_E$  improves stability but reduces available voltage for  $V_{CE}$  and output swing
  - Higher  $V_E$  improves stability but limits output swing

Suggest an optimization strategy for a battery-powered application where power consumption is critical versus a line-powered application where stability is paramount.

3. **Connection to Small-Signal Analysis:** The DC operating point established by the bias circuit determines the small-signal parameters. Research and briefly explain how the Q-point affects:

- Transconductance  $g_m = I_C/V_T$
- Input resistance  $r_\pi = \beta/g_m$
- Small-signal voltage gain

This foreshadows the next lab on small-signal amplifiers.