

Diode Applications: Rectifiers and Power Supplies

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

Diode Applications Overview

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

Why Study Rectifiers?:


- Most electronics need DC power
- Wall outlets provide AC power
- Rectifiers convert AC to DC
- Foundation of power supplies

Key Applications:

- Battery chargers
- Computer power supplies
- LED drivers
- Motor controllers

Topics We'll Cover:

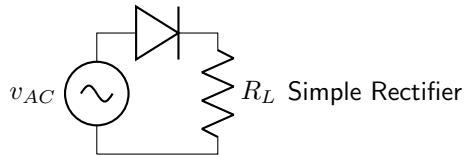- Half-wave rectifiers
- Full-wave rectifiers
- Bridge rectifiers
- Filtering capacitors
- Ripple voltage
- Voltage regulation with Zeners




Half-Wave Rectifier Circuit

ECEN 222

Maxx Seminario


Basic Circuit:

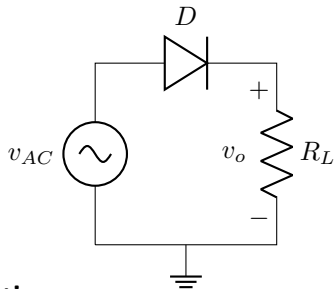

Operation:

- Input: $v_{AC} = V_p \sin(\omega t)$
- Positive half-cycle: diode ON
- Negative half-cycle: diode OFF
- Output: positive half-waves only

Waveforms:

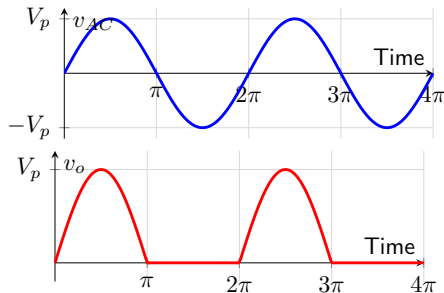

Half-Wave Rectifier Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Practical Considerations

Summary

Average (DC) Output Voltage:

For ideal diode ($V_D = 0$):

$$V_{DC} = \frac{V_p}{\pi} \approx 0.318V_p$$

For real silicon diode ($V_D \approx 0.7$ V):

$$V_{DC} = \frac{V_p - V_D}{\pi}$$

Peak Inverse Voltage (PIV):

- Maximum reverse voltage on diode
- $PIV = V_p$
- Must select diode with $PIV > V_p$

Example Calculation:

Given: $V_{AC,RMS} = 12$ V

- 1 Peak voltage:
 $V_p = \sqrt{2} \times V_{RMS} = 16.97$ V
- 2 Calculate DC output:
 $V_{DC} = \frac{16.97 - 0.7}{\pi} = \frac{16.27}{\pi} = 5.18$ V
- 3 PIV requirement:
 $PIV \geq 16.97$ V

Limitations:

- ☹ Low DC output (only 31.8%)
- ☹ Poor power utilization
- ☹ Large ripple voltage

Half-Wave Rectifier with Filter Capacitor

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers


Full-Wave Rectifiers

Voltage Regulation

Practical Considerations

Summary


Filtered Rectifier:

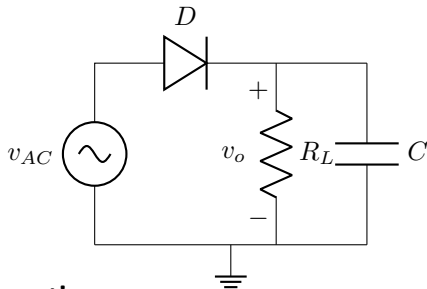

Operation:

- Capacitor charges to $\approx V_p$
- Capacitor discharges through R_L
- Creates "ripple" voltage
- DC voltage higher than unfiltered

Output Waveform:

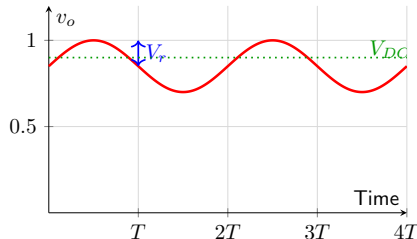

Ripple Voltage:

$$V_r \approx \frac{V_p}{fR_L C}$$

Ripple Voltage Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Practical Considerations

Summary

Key Equations:

Ripple voltage (peak-to-peak):

$$V_r \approx \frac{V_p}{f R_L C}$$

DC output voltage:

$$V_{DC} \approx V_p - \frac{V_r}{2}$$

Ripple factor:

$$r = \frac{V_{r,RMS}}{V_{DC}}$$

Design Guidelines:

- 😊 Larger C reduces ripple
- 😊 Larger R_L reduces ripple
- 😊 Higher frequency reduces ripple

Example:

Given:

- $V_p = 17 \text{ V}$
- $f = 60 \text{ Hz}$
- $R_L = 2.2 \text{ k}\Omega$
- $C = 470 \text{ }\mu\text{F}$

Calculate ripple:

$$V_r = \frac{17}{60 \times 2200 \times 470 \times 10^{-6}} = 0.274 \text{ V}$$

$$V_{DC} = 17 - \frac{0.274}{2} = 16.86 \text{ V}$$

Trade-offs:


- Large C : less ripple, larger size
- Peak diode current increases with C

Bridge Rectifier Circuit

ECEN 222

Maxx Seminario

Bridge Configuration:

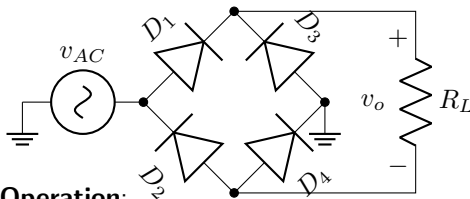

Operation:

- Positive half-cycle: D_1 , D_4 conduct
- Negative half-cycle: D_2 , D_3 conduct
- Both half-cycles produce output
- Two diodes always in series

Output Characteristics:

- v_o is always positive
- Output is full-wave rectified
- Continuous current through load

Advantages:

- 😊 No center-tap transformer needed
- 😊 Full-wave rectification
- 😊 Higher DC output
- 😊 Lower ripple frequency ($2f$)

Disadvantages:

- 😞 Two diode drops (≈ 1.4 V)
- 😞 Requires four diodes

Bridge Rectifier Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

DC Output Voltage:

For ideal diodes ($V_D = 0$):

$$V_{DC} = \frac{2V_p}{\pi} \approx 0.637V_p$$

For real silicon diodes ($V_D \approx 0.7$ V each):

$$V_{DC} = \frac{2(V_p - 2V_D)}{\pi}$$


Peak Inverse Voltage:

- Each diode: $PIV = V_p$
- Lower than center-tap configuration

Comparison to Half-Wave:

- DC output is 2x higher

Output Waveform:

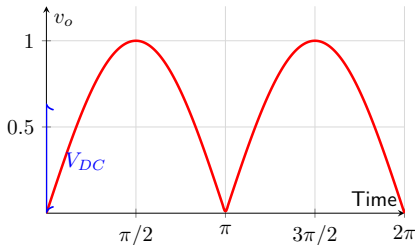

Example:

$V_{AC,RMS} = 12$ V, $V_p = 16.97$ V

$$V_{DC} = \frac{2(16.97 - 1.4)}{\pi} = \frac{31.14}{\pi} = 9.91 \text{ V}$$


Compare to half-wave: 5.18 V (nearly 2x)

Bridge Rectifier with Filter

ECEN 222

Maxx Seminario


Filtered Bridge Rectifier:

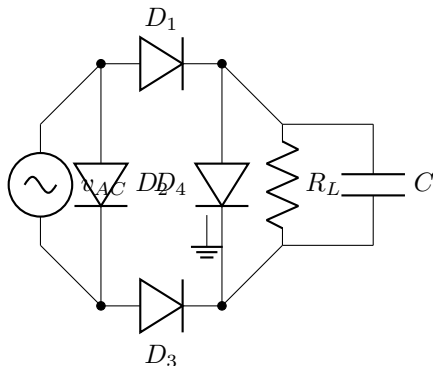

Key Difference:

Ripple frequency is $2f$ (120 Hz for 60 Hz)

Output Waveform:

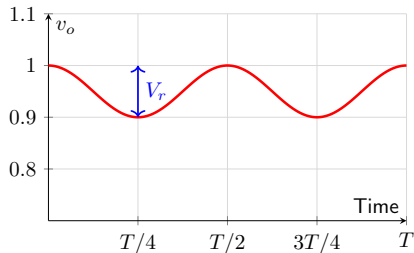

Design Example:

Same parameters as before, but $f \rightarrow 2f$:

$$V_r = \frac{17}{2 \times 60 \times 2200 \times 470 \times 10^{-6}} = \frac{17}{1.137} = 0.137 \text{ V}$$

Need for Voltage Regulation

ECEN 222

Maxx Seminario

The Problem:


- Rectifier output varies with:
 - Input (line) voltage changes
 - Load current changes
 - Ripple voltage
- Most circuits need stable DC
- Example: Logic circuits need $\pm 5\%$ tolerance

The Solution:

Voltage regulator:

- Maintains constant output voltage
- Compensates for input variations
- Compensates for load variations
- Types: Linear, switching, Zener

Block Diagram:

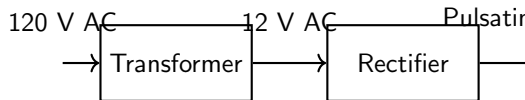

Performance Metrics:


- **Load regulation:** how much V_o changes with load
- **Line regulation:** how much V_o changes with input
- **Efficiency:** P_{out}/P_{in}

Zener Diode Shunt Regulator

ECEN 222

Maxx Seminario

Basic Shunt Regulator:

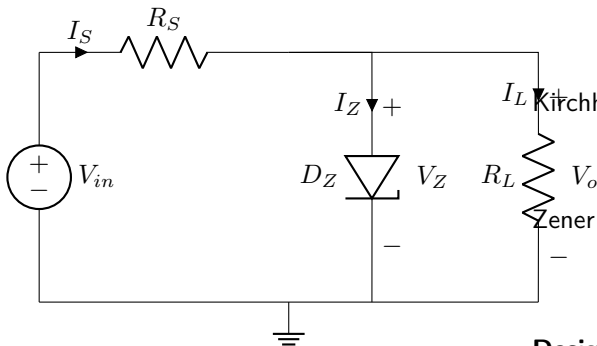

Operation Principle:

- Zener maintains constant V_Z

Key Equations:

Series resistor current:

$$I_S = \frac{V_{in} - V_Z}{R_S}$$

Kirchhoff's current law:

$$I_Z = I_S - I_L$$

Zener power dissipation:

$$P_Z = V_Z \cdot I_Z$$

Design Constraints:

- $I_Z \geq I_{Z,min}$ (stay in breakdown)
- $P_Z \leq P_{Z,max}$ (power rating)

Shunt Regulator Design Example

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

Design Specifications:

- Output: $V_o = 5.1$ V (use 5.1 V Zener)
- Input: $V_{in} = 12$ V (from filtered rectifier)
- Load: $I_L = 0$ to 50 mA
- Zener: $I_{Z,min} = 5$ mA, $P_{Z,max} = 500$ mW

Design Process:

Step 1: Choose I_S at no-load

Let $I_S = 2 \times I_{L,max} = 100$ mA

This ensures enough current for regulation

Step 2: Calculate R_S

$$R_S = \frac{V_{in} - V_Z}{I_S} = \frac{12 - 5.1}{0.1} = 69 \Omega$$

Step 3: Verify worst-case conditions

At no load ($I_L = 0$):

$$I_Z = I_S - I_L = 100 - 0 = 100 \text{ mA}$$

$$P_Z = 5.1 \times 0.1 = 510 \text{ mW}$$

Problem! Exceeds 500 mW rating

Step 4: Redesign with lower I_S

Maximum safe I_Z :

$$I_{Z,max} = \frac{P_{Z,max}}{V_Z} = \frac{0.5}{5.1} = 98 \text{ mA}$$

Choose $I_S = I_{Z,max} = 98$ mA, then:

$$R_S = \frac{12 - 5.1}{0.098} = 70.4 \Omega$$

Regulation Performance

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

Load Regulation:

Measures output voltage change with load current:

$$\text{Load Reg} = \frac{V_{o,\text{no-load}} - V_{o,\text{full-load}}}{V_{o,\text{full-load}}} \times 100\%$$

Affected by:

- Zener dynamic resistance r_z
- Series resistance R_S
- Load current range

Line Regulation:

Measures output voltage change with input voltage:

Efficiency:

$$\eta = \frac{P_o}{P_{in}} = \frac{V_o I_L}{V_{in} I_S} \times 100\%$$

Example (from previous design):

At full load ($I_L = 50 \text{ mA}$):

$$P_o = 5.1 \times 0.050 = 0.255 \text{ W}$$

$$P_{in} = 12 \times 0.098 = 1.176 \text{ W}$$

$$\eta = \frac{0.255}{1.176} = 21.7\%$$

Key Points:

- ☹ Shunt regulators have poor efficiency
- ☹ Power wasted in R_S and Zener
- 😊 Simple and inexpensive

Component Selection

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

Diode Selection:

Key ratings:

- **PIV rating:** Must exceed peak voltage with safety margin (2x)
- **Average current:** Must handle DC load current
- **Peak current:** Can be 10x average for capacitive loads
- **Forward voltage:** Lower is better for efficiency

Common types:

- 1N4001-1N4007 series (1A, 50V-1000V)
- Fast recovery for high frequency
- Schottky for low voltage drop

Safety Considerations:

- Capacitors store charge—discharge before handling
- Use fuses for overcurrent protection
- Heat sinks for high-power diodes
- Proper grounding essential

Common Mistakes:

- ☹ Reversed diode polarity
- ☹ Reversed capacitor polarity
- ☹ Undersized PIV rating
- ☹ Insufficient heat sinking
- ☹ Forgetting safety margin

Testing Tips:

Summary: Diode Applications

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Practical
Considerations

Summary

Rectifier Circuits:

Half-Wave:

- $V_{DC} = V_p/\pi \approx 0.318V_p$
- $PIV = V_p$
- Ripple frequency = f
- Low efficiency

Bridge (Full-Wave):

- $V_{DC} = 2V_p/\pi \approx 0.637V_p$
- $PIV = V_p$ (per diode)
- Ripple frequency = $2f$
- Better efficiency

Filtering:

- Capacitor smooths output

Voltage Regulation:

Zener Shunt Regulator:

- Maintains constant output
- $I_S = I_Z + I_L$
- $R_S = (V_{in} - V_Z)/I_S$
- Check power dissipation

Performance:

- Load regulation: ΔV_o with ΔI_L
- Line regulation: ΔV_o with ΔV_{in}
- Efficiency: typically poor (20-50%)

Next Topics:

- Transistor fundamentals
- MOS transistors