

MOSFET DC Analysis and Biasing

Unit 5: Field-Effect Transistors

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

Lecture Overview

Review from Last Lecture

- MOSFET device structure
- Operating regions (cutoff, linear, saturation)
- I-V characteristics
- Field effect and channel modulation

Learning Objectives

- Analyze MOSFET DC circuits
- Determine Q-point for different bias configurations
- Design bias circuits for specified operating points

DC Operating Point (Q-Point)

What is the Q-Point?

- Quiescent operating point
- DC voltages and currents with no signal
- Determines transistor operating region


Q-Point Parameters:

- V_{GS} : Gate-source voltage
- V_{DS} : Drain-source voltage
- I_{DS} : Drain-source current

Design Goals:

- Ensure proper operating region
- Maximize voltage swing
- Minimize power consumption

Q-Point on I-V Characteristics

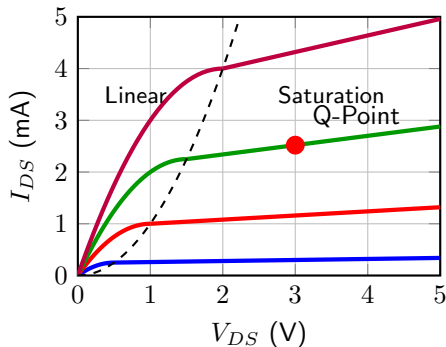

Key Concept

The Q-point sets the DC bias, determining where the transistor operates and its 'behavior / character'.

DC Analysis General Procedure

1 Assume an operating region

2 Apply KVL and KCL to the circuit

- Use DC voltage sources only (capacitors open, inductors short)
- Write node and loop equations

3 Apply MOSFET equations for the assumed region

- Saturation: $I_D = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th})^2$
- Linear: $I_D = \mu_n C_{ox} \frac{W}{L} \left[(V_{GS} - V_{th})V_{DS} - \frac{V_{DS}^2}{2} \right]$
- Cutoff: $I_D = 0$


4 Solve for unknowns: V_{GS} , V_{DS} , I_D

5 Verify the assumption from step 1

- Saturation: Check $V_{DS} \geq V_{GS} - V_{th}$ and $V_{GS} > V_{th}$
- Linear: Check $V_{DS} < V_{GS} - V_{th}$ and $V_{GS} > V_{th}$
- If violated, re-analyze with correct region

Fixed Gate Bias Configuration

Circuit Schematic

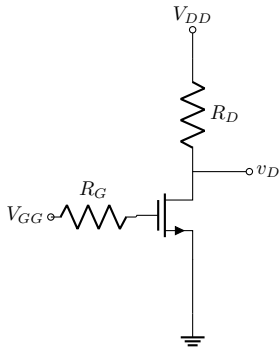

DC Analysis:

Given: V_{DD} , V_{GG} , R_D , R_G , V_{th} , $k_n = \frac{1}{2}\mu_n C_{ox} \frac{W}{L}$

Step 1: Gate-source voltage (assume $I_G = 0$)

$$V_{GS} = V_G - V_S = V_{GG}$$

Step 2: Drain current (assuming saturation)

$$I_D = k_n(V_{GS} - V_{th})^2 = k_n(V_{GG} - V_{th})^2$$

Step 3: Drain voltage (KVL)


$$V_{DS} = V_D - V_S = V_{DD} - I_D R_D$$

Step 7: Verify saturation (our previous assumption)

$$V_{DS} \geq V_{GS} - V_{th}$$

Voltage Divider Bias Configuration

Circuit Diagram

 

- Most common biasing method
- Best stability
- Independent of device parameters if designed properly

DC Analysis: Gate and Source voltages

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}, \quad V_S = I_D R_S$$
$$V_{GS} = V_G - V_S = V_{DD} \frac{R_2}{R_1 + R_2} - I_D R_S$$

Drain current (assume saturation)

$$I_D = k_n (V_{GS} - V_{th})^2$$

Substitute and solve quadratic for I_D .

Drain-Source voltage

$$V_D = V_{DD} - I_D R_D,$$

$$V_{DS} = V_D - V_S = V_{DD} - I_D (R_D + R_S)$$

Design Considerations for DC Biasing

Operating Region

- For amplifiers: saturation region
- Ensure $V_{DS} \geq V_{GS} - V_{th}$

Voltage Swing

- Maximize output voltage range
- Center Q-point on load line
- Typical: $V_{DS} \approx \frac{V_{DD}}{2}$

Power Dissipation

- $P_D = V_{DS} \cdot I_D$
- Consider thermal limits
- Trade-off with performance

Component Selection

- Consider tolerances
- Power ratings for resistors

Design Steps

- 1 Choose I_D based on application
- 2 Set V_{DS} for desired swing
- 3 Calculate required V_{GS}
- 4 Design bias network
- 5 Verify operation through simulation

Example: Voltage Divider Bias Design

Given:

- $V_{DD} = 12\text{ V}$
- $V_{th} = 1\text{ V}$
- $k_n = 2\text{ mA/V}^2$
- Design for: $I_D = 2\text{ mA}$, $V_{DS} = 6\text{ V}$

Step 1: Choose V_S (Artist's choice)

$$V_S = 2\text{ V}$$

Step 2: Calculate R_S , V_D

$$R_S = \frac{V_S}{I_D} = \frac{2}{2 \times 10^{-3}} = 1\text{ k}\Omega$$

$$V_D = V_S + V_{DS} = 2 + 6 = 8\text{ V}$$

Step 3: Calculate R_D

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{12 - 8}{2 \times 10^{-3}} = 2\text{ k}\Omega$$

Step 4: Find required V_{GS} (assume saturation)

$$I_D = k_n(V_{GS} - V_{th})^2$$

$$2 = 2(V_{GS} - 1)^2$$

$$V_{GS} = 2\text{ V} \quad V_G = 4\text{ V}$$

Step 6: Design voltage divider

$$\frac{R_2}{R_1 + R_2} = \frac{V_G}{V_{DD}} = \frac{4}{12} = \frac{1}{3}$$

$$R_2 = 20\text{ k}\Omega, \quad R_1 = 40\text{ k}\Omega$$