

# Diode Applications: Rectifiers and Power Supplies

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

# Diode Applications Overview

ECEN 222

Maxx Seminario

Introduction

Half-Wave  
Rectifiers

Full-Wave  
Rectifiers

Voltage  
Regulation

Summary

## Why Study Rectifiers?:


- Most electronics need DC power
- Wall outlets provide AC power
- Rectifiers convert AC to DC
- Foundation of power supplies

## Key Applications:

- Battery chargers
- Computer power supplies
- LED drivers
- Motor controllers
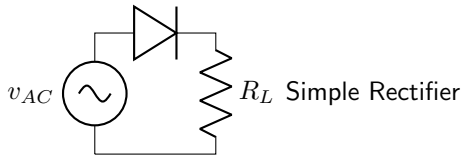
## Topics We'll Cover:

- Half-wave rectifiers
- Full-wave rectifiers
- Bridge rectifiers
- Filtering capacitors
- Ripple voltage
- Voltage regulation with Zeners




# Half-Wave Rectifier Circuit

ECEN 222

Maxx Seminario


## Basic Circuit:

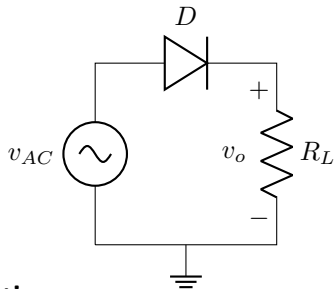

## Operation:

- Input:  $v_{AC} = V_p \sin(\omega t)$
- Positive half-cycle: diode ON
- Negative half-cycle: diode OFF
- Output: positive half-waves only

## Waveforms:

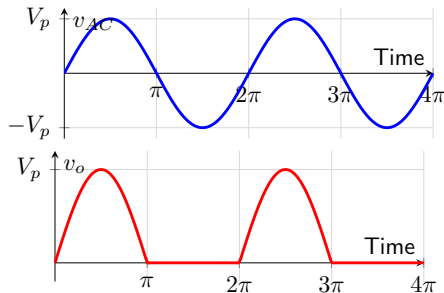

# Half-Wave Rectifier Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Summary

## Average (DC) Output Voltage:

For ideal diode ( $V_D = 0$ ):

$$V_{DC} = \frac{V_p}{\pi} \approx 0.318V_p$$

For real silicon diode ( $V_D \approx 0.7$  V):

$$V_{DC} = \frac{V_p - V_D}{\pi}$$

## Peak Inverse Voltage (PIV):

- Maximum reverse voltage on diode
- Must select diode with  $PIV > V_p$
- Else, diode may break down during negative half-cycle

## Example Calculation:

Given:  $V_{AC,RMS} = 12$  V

- 1 Peak voltage:  
 $V_p = \sqrt{2} \times V_{RMS} = 17$  V
- 2 Calculate DC output:  
 $V_{DC} = \frac{17-0.7}{\pi} = \frac{16.27}{\pi} = 5.18$  V
- 3 PIV requirement:  
 $PIV \geq 17$  V

## Limitations:

- ☹ Low DC output (only 31.8%)
- ☹ Poor power utilization
- ☹ Large ripple voltage

# Half-Wave Rectifier with Filter Capacitor

ECEN 222

Maxx Seminario

Introduction


Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Summary


## Filtered Rectifier:

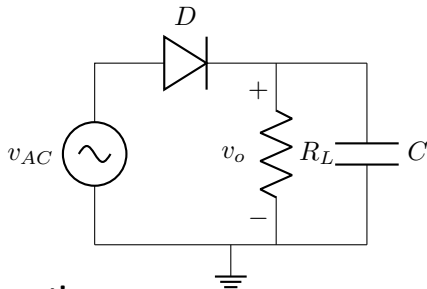

## Operation:

- Capacitor charges to  $\approx V_p$
- Capacitor discharges through  $R_L$
- Creates "ripple" voltage
- DC voltage higher than unfiltered

## Output Waveform:

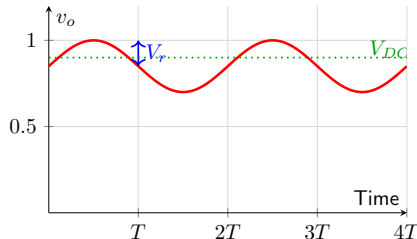

## Ripple Voltage:

$$V_r \approx \frac{V_p}{fR_L C}$$

# Ripple Voltage Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Summary

## Key Equations:

Ripple voltage (peak-to-peak):

$$V_r \approx \frac{V_p}{f R_L C}$$

DC output voltage:

$$V_{DC} \approx V_p - \frac{V_r}{2}$$

Ripple factor:

$$r = \frac{V_{r,RMS}}{V_{DC}}$$

## Design Guidelines:

- 😊 Larger  $C$  reduces ripple
- 😊 Larger  $R_L$  reduces ripple
- 😊 Higher frequency reduces ripple

## Example:

Given:

- $V_p = 17 \text{ V}$
- $f = 60 \text{ Hz}$
- $R_L = 2.2 \text{ k}\Omega$
- $C = 470 \text{ }\mu\text{F}$

Calculate ripple:

$$V_r = \frac{17}{60 \times 2200 \times 470 \times 10^{-6}} = 0.274 \text{ V}$$

$$V_{DC} = 17 - \frac{0.274}{2} = 16.86 \text{ V}$$

## Trade-offs:


- Large  $C$ : less ripple, larger size
- Peak diode current increases with  $C$

# Bridge Rectifier Circuit

ECEN 222

Maxx Seminario

## Bridge Configuration:

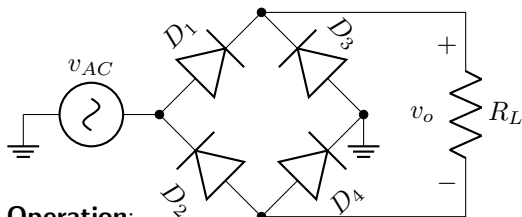

## Operation:

- Positive half-cycle:  $D_1, D_4$  conduct
- Negative half-cycle:  $D_2, D_3$  conduct
- Both half-cycles produce output
- Two diodes always in series

## Output Characteristics:

- $v_o$  is always positive
- Output is full-wave rectified
- Continuous current through load

## Advantages:

- 😊 No center-tap transformer needed
- 😊 Full-wave rectification
- 😊 Higher DC output
- 😊 Lower ripple frequency ( $2f$ )

## Disadvantages:

- 😞 Two diode drops ( $\approx 1.4 \text{ V}$ )
- 😞 Requires four diodes

# Bridge Rectifier Analysis

ECEN 222

Maxx Seminario

## DC Output Voltage:

For ideal diodes ( $V_D = 0$ ):

$$V_{DC} = \frac{2V_p}{\pi} \approx 0.637V_p$$


For real silicon diodes ( $V_D \approx 0.7$  V each):

$$V_{DC} = \frac{2(V_p - 2V_D)}{\pi}$$

## Comparison to Half-Wave:

- DC output is 2x higher
- Ripple frequency is 2x higher
- Better power utilization

## Output Waveform:

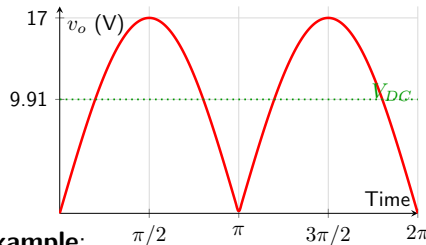

### Example:

$$V_{AC,RMS} = 12 \text{ V}, V_p = 17 \text{ V}$$

$$V_{DC} = \frac{2(17 - 1.4)}{\pi} = \frac{31.14}{\pi} = 9.91 \text{ V}$$

Compare to half-wave: 5.18 V (nearly 2x improvement!)




# Bridge Rectifier with Filter

ECEN 222

Maxx Seminario

## Filtered Bridge Rectifier:

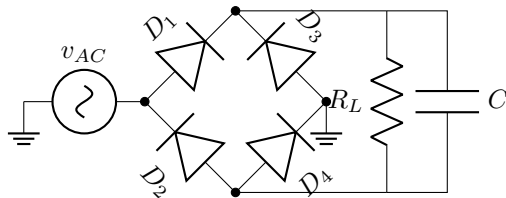


### Key Difference:

Ripple frequency is  $2f$

$$V_r \approx \frac{V_p}{2fR_L C}$$

Ripple is **half** that of half-wave rectifier with same  $C$ !

## Output Waveform:

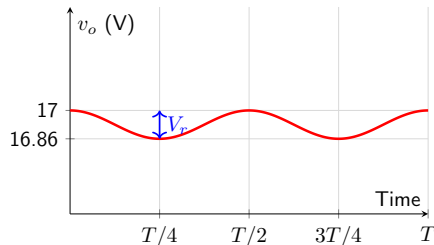

### Design Example:

Same parameters as before, but  $f \rightarrow 2f$ :

$$V_r = \frac{17}{2 \times 60 \times 2200 \times 470 \times 10^{-6}} = 0.137 \text{ V}$$

$$V_{DC} = 17 - \frac{0.137}{2} = 16.93 \text{ V}$$

# Need for Voltage Regulation

ECEN 222

Maxx Seminario

Introduction

Half-Wave  
Rectifiers

Full-Wave  
Rectifiers

Voltage  
Regulation

Summary

## The Problem:

- Rectifier output varies with:
  - Input voltage changes
  - Load current changes
  - Ripple voltage
- Most circuits need stable DC
- Example: Logic circuits need  $\pm 5\%$  tolerance

## The Solution:

Voltage regulator:

- Maintains constant output voltage
- Compensates for input variations
- Compensates for load variations
- Types: Linear, switching, Zener

## Performance Metrics:


- **Load regulation:** how much  $V_o$  changes with load
- **Line regulation:** how much  $V_o$  changes with input
- **Efficiency:**  $P_{out}/P_{in}$

# Zener Diode Shunt Regulator

ECEN 222

Maxx Seminario

## Basic Shunt Regulator:

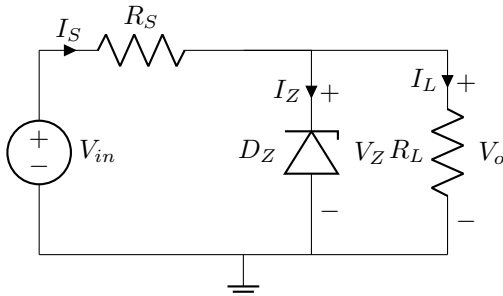

## Operation Principle:

- Zener maintains constant  $V_Z$
- $R_S$  drops excess voltage
- Zener absorbs current variations
- $I_S = I_Z + I_L$  (KCL)

## Equations of Note:

Series resistor current:

$$I_S = \frac{V_{in} - V_Z}{R_S}$$

Kirchhoff's current law:

$$I_Z = I_S - I_L$$

Zener power dissipation:

$$P_Z = V_Z \cdot I_Z$$

## Design Constraints:

- $I_Z \geq I_{Z,min}$  (stay in breakdown)
- $P_Z \leq P_{Z,max}$  (power rating)
- Worst case: max  $I_L$ , min  $V_{in}$
- Best efficiency at full load

# Shunt Regulator Design Example

ECEN 222

Maxx Seminario

Introduction

Half-Wave  
Rectifiers

Full-Wave  
Rectifiers

Voltage  
Regulation

Summary

## Design Specifications:

- Output:  $V_o = 5.1 \text{ V}$  (use 5.1 V Zener)
- Input:  $V_{in} = 12 \text{ V}$  (from rectifier)
- Load:  $I_L = 0$  to 50 mA
- Zener:  $I_{Z,min} = 5 \text{ mA}$ ,  $P_{Z,max} = 0.5 \text{ W}$

## Design Process:

**Step 1:** Find maximum safe  $I_Z$

$$I_{Z,max} = \frac{P_{Z,max}}{V_Z} = \frac{0.5}{5.1} = 98 \text{ mA}$$

**Step 2:** Choose  $I_S$  for no-load condition:

At no load,  $I_Z = I_S$ , so choose  $I_S = 90 \text{ mA}$  (safe margin below 98 mA)

**Step 3:** Calculate  $R_S$

$$R_S = \frac{V_{in} - V_Z}{I_S} = \frac{12 - 5.1}{0.09} = 76.7 \Omega$$

**Step 4:** Verify operation at both extremes  
At no load ( $I_L = 0$ ):

$$I_Z = I_S = 90 \text{ mA}$$

$$P_Z = 5.1 \times 0.09 = 459 \text{ mW}$$

At full load ( $I_L = 50 \text{ mA}$ ):

$$I_Z = 90 - 50 = 40 \text{ mA}$$

$$> I_{Z,min} = 5 \text{ mA}$$

# Regulation Performance

ECEN 222

Maxx Seminario

Introduction

Half-Wave  
Rectifiers

Full-Wave  
Rectifiers

Voltage  
Regulation

Summary

## Load Regulation:

Measures output voltage change with load current:

$$\text{Load Reg} = \frac{V_{o,no-load} - V_{o,full-load}}{V_{o,full-load}} \times 100\%$$

Affected by:

- Zener dynamic resistance  $r_z$
- Series resistance  $R_S$
- Load current range

## Line Regulation:

Measures output voltage change with input voltage:

$$\text{Line Reg} = \frac{\Delta V_o}{\Delta V_{in}} \times 100\%$$

## Efficiency:

$$\eta = \frac{P_o}{P_{in}} = \frac{V_o I_L}{V_{in} I_S} \times 100\%$$

## Key Points:

- ☹ Shunt regulators have poor efficiency
- ☹ Power wasted in  $R_S$  and Zener
- 😊 Simple and inexpensive
- 😊 Good for low-power applications

# Summary: Diode Applications

ECEN 222

Maxx Seminario

Introduction

Half-Wave  
Rectifiers

Full-Wave  
Rectifiers

Voltage  
Regulation

Summary

## Rectifier Circuits:

### Half-Wave:

- $V_{DC} = V_p/\pi \approx 0.318V_p$
- Ripple frequency =  $f$
- Low efficiency

### Bridge (Full-Wave):

- $V_{DC} = 2V_p/\pi \approx 0.637V_p$
- Ripple frequency =  $2f$
- Better efficiency

### Filtering:

- Capacitor smooths output
- $V_r \approx V_p/(fR_LC)$
- Larger  $C$  reduces ripple

## Voltage Regulation:

### Zener Shunt Regulator:

- Maintains constant output
- $I_S = I_Z + I_L$
- $R_S = (V_{in} - V_Z)/I_S$
- Check power dissipation

### Performance:

- Load regulation:  $\Delta V_o$  with  $\Delta I_L$
- Line regulation:  $\Delta V_o$  with  $\Delta V_{in}$
- Efficiency: typically 20-50%