

# MOSFET AC Analysis and Small-Signal Models

## Unit 5: Field-Effect Transistors

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

# AC vs DC Analysis


## DC Analysis

- Establishes Q-point
- Determines operating region
- Uses large-signal model
- Static voltages and currents

## AC Analysis

- Small variations around Q-point
- Uses small-signal model
- Linear approximation
- Frequency-dependent behavior

Total Signal = DC + AC

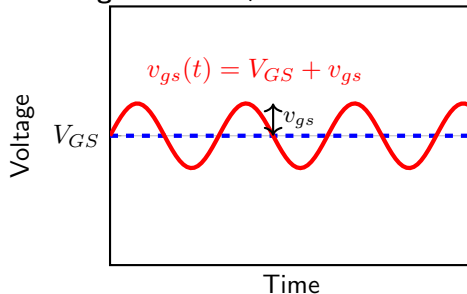

### Key Concept

AC analysis assumes small signals ( $v_{gs} \ll V_{GS}$ ), allowing linear approximation around the Q-point.

# Small-Signal Linearization

## Nonlinear DC Relationship

$$i_D = k_n(v_{GS} - V_{th})^2(1 + \lambda v_{DS})$$

## Total signals:

$$v_{GS}(t) = V_{GS} + v_{gs}(t)$$

$$v_{DS}(t) = V_{DS} + v_{ds}(t)$$


$$i_D(t) = I_D + i_d(t)$$

## Taylor Series Expansion

$$i_D(t) = I_D + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q v_{gs} + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q v_{ds} + \dots$$

For small signals, higher-order terms negligible.

## Graphical Interpretation

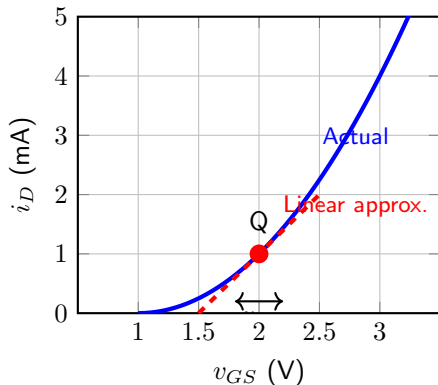

Slope at Q-point = transconductance  $g_m$

# Common Source Amplifier: Voltage Gain Mechanism

## Small Changes in $V_{GS}$ Create Large Changes in $V_{DS}$


Consider a common source amplifier biased at Q-point:

- Input signal varies  $v_{GS}$
- This modulates drain current  $i_D$
- Current flows through load resistor  $R_D$
- Output voltage  $v_{DS}$  changes

### Voltage Gain

Small  $\Delta v_{GS} \Rightarrow$  Large  $\Delta i_D \Rightarrow$  Large  $\Delta v_{DS}$   
This is the fundamental amplification mechanism.

## Voltage Transfer Characteristic (VTC)

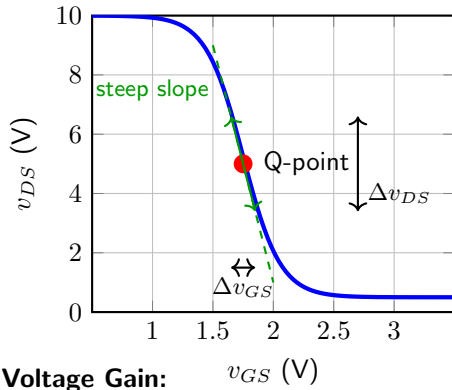

**Voltage Gain:**  $v_{GS}$  (V)

$$A_v = \frac{\Delta v_{DS}}{\Delta v_{GS}} = \text{slope of VTC}$$

# Transconductance $g_m$

## Definition

Transconductance relates small-signal gate voltage to drain current:

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q$$

## Derivation (Saturation, no CLM)

$$I_D = k_n (V_{GS} - V_{th})^2$$

$$g_m = \frac{\partial}{\partial V_{GS}} [k_n (V_{GS} - V_{th})^2]$$

$$g_m = 2k_n (V_{GS} - V_{th}) = 2k_n V_{OV}$$

where  $V_{OV} = V_{GS} - V_{th}$ , overdrive voltage.

## Alternative Forms

Since  $I_D = k_n V_{OV}^2$ , we can write:

$$g_m = \sqrt{2k_n I_D} = \frac{2I_D}{V_{OV}}$$

**Units:** mA/V or mS (millisiemens)

## Physical Interpretation

- 😊 Voltage-to-current gain
- 😊 Larger  $g_m$  = better amplification
- 😊 Increases with  $I_D$  and device size ( $W/L$ )
- 😞 Decreases with  $V_{OV}$  (for fixed  $I_D$ )

## Important

$g_m$  is determined by the DC operating point

# Output Resistance $r_o$ - Channel Length Modulation

## Channel-Length Modulation (CLM)

In saturation,  $I_D$  depends slightly on  $V_{DS}$ :

$$I_D = k_n(V_{GS} - V_{th})^2(1 + \lambda V_{DS})$$

where  $\lambda$  is the CLM parameter ( $V^{-1}$ ).

## Output Resistance


$$r_o = \left. \frac{\partial v_{DS}}{\partial i_D} \right|_Q$$

## Derivation:

$$\frac{\partial i_D}{\partial v_{DS}} = k_n(V_{GS} - V_{th})^2 \lambda = \lambda I_D$$

$$r_o = \frac{1}{\lambda I_D}$$

## I-V Curves with CLM

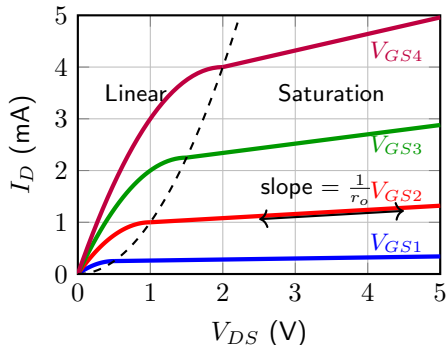


## Typical Values

- $\lambda = 0.01$  to  $0.1 \text{ V}^{-1}$
- $r_o = 10$  to  $100 \text{ k}\Omega$
- 😊 Higher  $r_o$  = better current source

# MOSFET Small-Signal Equivalent Circuit

## Small-Signal Model (Saturation)

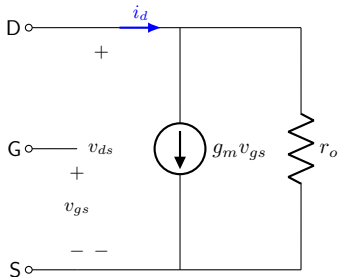

### Key Features:

- Voltage-controlled current source
- Infinite input resistance (DC/low freq)
- Finite output resistance  $r_o$

## Small-Signal Parameters

Parameter	Expression
$g_m$	$2k_n V_{OV} = \sqrt{2k_n I_D}$
$r_o$	$\frac{1}{\lambda I_D}$
$i_d$	$g_m v_{gs} + \frac{v_{ds}}{r_o}$

### Simplified Model ( $r_o \rightarrow \infty$ / $\lambda = 0$ )

$$i_d = g_m v_{gs}$$

The small-signal model is only valid for:

- Small signal amplitudes
- Frequencies where capacitances can be ignored
- Operation in saturation region

## Example: Small-Signal Parameter Calculation

### Given DC Operating Point:

- $V_{GS} = 2 \text{ V}$
- $V_{DS} = 6 \text{ V}$
- $I_D = 2 \text{ mA}$
- $V_{th} = 1 \text{ V}$
- $k_n = 2 \text{ mA/V}^2$
- $\lambda = 0.02 \text{ V}^{-1}$

**Find:**  $g_m$  and  $r_o$

**Solution:**

**Step 1:** Calculate overdrive voltage

$$V_{OV} = V_{GS} - V_{th} = 2 - 1 = 1 \text{ V}$$

**Step 2:** Calculate transconductance

Using  $g_m = 2k_n V_{OV}$ :

$$g_m = 2 \times 2 \times 1 = 4 \text{ mA/V}$$

**Step 3:** Calculate output impedance

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{0.02 \times 2 \times 10^{-3}} = \frac{1}{4 \times 10^{-5}}$$

$r_o = 25 \text{ k}\Omega$

**Result:** Small-signal model has  $g_m = 4 \text{ mA/V}$  and  $r_o = 25 \text{ k}\Omega$ .



# AC Analysis Procedure

## 1 Perform DC Analysis

- Find Q-point:  $V_{GS}$ ,  $V_{DS}$ ,  $I_D$
- Verify operating region

## 2 Calculate Small-Signal Parameters

- $g_m = 2k_n V_{OV}$  or  $g_m = \sqrt{2k_n I_D}$
- $r_o = \frac{1}{\lambda I_D}$  (if CLM included)

## 3 Draw AC Equivalent Circuit

- Replace MOSFET with small-signal model
- DC sources  $\rightarrow$  ground (short circuit)
- Capacitors  $\rightarrow$  short circuit (at high frequencies)
- DC biasing resistors remain

## 4 Analyze AC Circuit


- Apply KVL, KCL, Ohm's law
- Calculate voltage gain, input/output impedance

### Key Point

Always perform DC analysis first to establish the Q-point before conducting AC analysis.

# Example: Common Source Amplifier Analysis


## DC Circuit

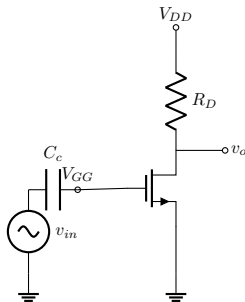

### Given:

- $R_D = 2 \text{ k}\Omega$
- $g_m = 4 \text{ mA/V}$
- $r_o = 25 \text{ k}\Omega$


## AC Equivalent Circuit

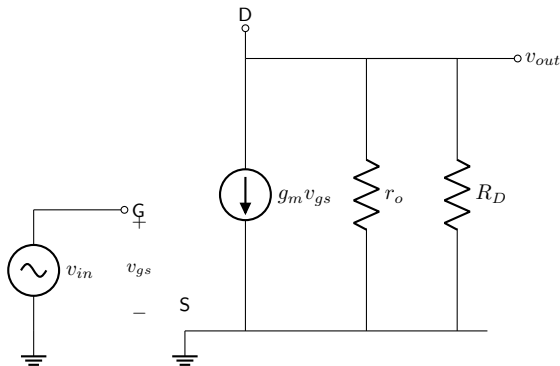

### Analysis:

$$v_{gs} = v_{in} \text{ (ideal coupling)}$$
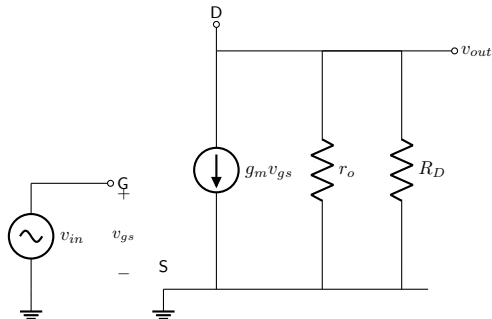
## Example: Common Source Amplifier - Small-Signal Analysis



**Given:**

- $R_D = 2 \text{ k}\Omega$
- $g_m = 4 \text{ mA/V}$
- $r_o = 25 \text{ k}\Omega$

**Small-Signal Analysis:**

**Current**  $i_d$  from controlled source

$$i_d = g_m v_{gs} = g_m v_{in}$$

**Output voltage** (KVL at drain node)

Current flows through  $R_D \parallel r_o$ :

$$v_{out} = -i_d(R_D \parallel r_o) = -g_m v_{in}(R_D \parallel r_o)$$

$$A_v = \frac{v_{out}}{v_{in}} = -g_m(R_D \parallel r_o)$$

$$R_D \parallel r_o = \frac{2 \times 25}{2 + 25} = 1.85 \text{ k}\Omega$$

$$A_v = -4 \times 1.85 = -7.4$$

# Impact of Output Resistance on Gain

## Voltage Gain with CLM

$$A_v = -g_m(R_D \parallel r_o) = -g_m \frac{R_D r_o}{R_D + r_o}$$

### Two Limiting Cases:

**Case 1:**  $r_o \gg R_D$  (ideal case)

$$A_v \approx -g_m R_D$$


Maximum achievable gain.

**Case 2:**  $r_o \ll R_D$  (high CLM)

$$A_v \approx -g_m r_o = -\frac{g_m}{\lambda I_D}$$

Gain limited by device physics.

## Gain vs. $r_o$

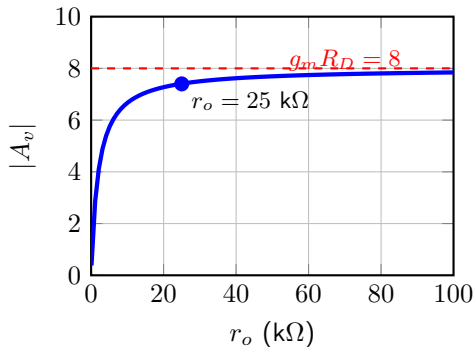

## Design Insight:

- 😊 Higher  $r_o$  improves gain
- 😊 Long-channel devices have higher  $r_o$

# Summary: MOSFET Small-Signal Parameters

Parameter	Definition	Formula	Typical Value
Transconductance	$\frac{\partial i_D}{\partial v_{GS}}$	$g_m = 2k_n V_{OV} = \sqrt{2k_n I_D}$	1-10 mA/V
Output resistance	$\frac{\partial v_{DS}}{\partial i_D}$	$r_o = \frac{1}{\lambda I_D}$	10-100 k $\Omega$
Body transconductance	$\frac{\partial i_D}{\partial v_{BS}}$	$g_{mb} = \eta g_m$	0.1-0.3 $g_m$

## Key Relationships:

- $g_m \propto \sqrt{I_D}$
- $g_m \propto \sqrt{W/L}$
- $r_o \propto 1/I_D$
- $g_m \cdot r_o = \frac{2}{\lambda V_{OV}}$  (intrinsic gain)

## Design Trade-offs:

- Large  $I_D \Rightarrow$  high  $g_m$ , low  $r_o$
- Large  $W/L \Rightarrow$  high  $g_m$ , more area
- Small  $V_{OV} \Rightarrow$  high  $g_m$  (for given  $I_D$ )
- Long channel  $\Rightarrow$  small  $\lambda$ , high  $r_o$