

Diode Applications: Rectifiers and Power Supplies

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

Diode Applications Overview

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

Why Study Rectifiers?:


- Most electronics need DC power
- Wall outlets provide AC power
- Rectifiers convert AC to DC
- Foundation of power supplies

Key Applications:

- Battery chargers
- Computer power supplies
- LED drivers
- Motor controllers

Topics We'll Cover:

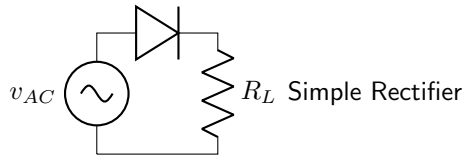- Half-wave rectifiers
- Full-wave rectifiers
- Bridge rectifiers
- Filtering capacitors
- Ripple voltage
- Voltage regulation with Zeners




Half-Wave Rectifier Circuit

ECEN 222

Maxx Seminario


Basic Circuit:

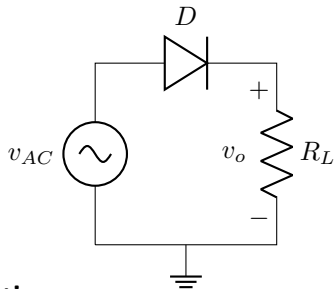

Operation:

- Input: $v_{AC} = V_p \sin(\omega t)$
- Positive half-cycle: diode ON
- Negative half-cycle: diode OFF
- Output: positive half-waves only

Waveforms:

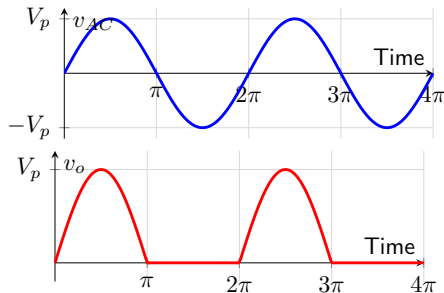

Half-Wave Rectifier Analysis

ECEN 222

Maxx Seminario

Average (DC) Output Voltage:

For ideal diode ($V_D = 0$):

$$V_{DC} = \frac{V_p}{\pi} \approx 0.318V_p$$

For real silicon diode ($V_D \approx 0.7$ V):

$$V_{DC} = \frac{V_p - V_D}{\pi}$$

Peak Inverse Voltage (PIV):

- Maximum reverse voltage on diode
- Must select diode with $PIV > V_p$
- Else, diode may break down during negative half-cycle

Example Calculation:

Given: $V_{AC,RMS} = 12$ V

- 1 Peak voltage:
 $V_p = \sqrt{2} \times V_{RMS} = 17$ V
- 2 Calculate DC output:
 $V_{DC} = \frac{17-0.7}{\pi} = \frac{16.27}{\pi} = 5.18$ V
- 3 PIV requirement:
 $PIV \geq 17$ V

Limitations:

- ☹ Low DC output (only 31.8%)
- ☹ Poor power utilization
- ☹ Large ripple voltage

Half-Wave Rectifier with Filter Capacitor

ECEN 222

Maxx Seminario

Introduction


Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Summary


Filtered Rectifier:

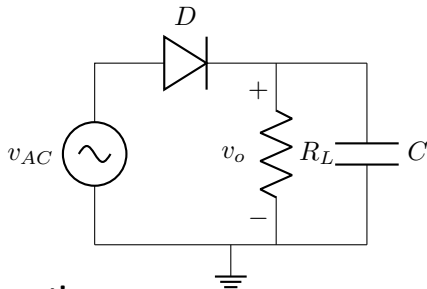

Operation:

- Capacitor charges to $\approx V_p$
- Capacitor discharges through R_L
- Creates "ripple" voltage
- DC voltage higher than unfiltered

Output Waveform:

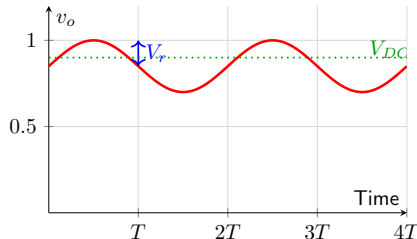

Ripple Voltage:

$$V_r \approx \frac{V_p}{fR_L C}$$

Ripple Voltage Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave Rectifiers

Full-Wave Rectifiers

Voltage Regulation

Summary

Key Equations:

Ripple voltage (peak-to-peak):

$$V_r \approx \frac{V_p}{f R_L C}$$

DC output voltage:

$$V_{DC} \approx V_p - \frac{V_r}{2}$$

Ripple factor:

$$r = \frac{V_{r,RMS}}{V_{DC}}$$

Design Guidelines:

- 😊 Larger C reduces ripple
- 😊 Larger R_L reduces ripple
- 😊 Higher frequency reduces ripple

Example:

Given:

- $V_p = 17 \text{ V}$
- $f = 60 \text{ Hz}$
- $R_L = 2.2 \text{ k}\Omega$
- $C = 470 \text{ }\mu\text{F}$

Calculate ripple:

$$V_r = \frac{17}{60 \times 2200 \times 470 \times 10^{-6}} = 0.274 \text{ V}$$

$$V_{DC} = 17 - \frac{0.274}{2} = 16.86 \text{ V}$$

Trade-offs:


- Large C : less ripple, larger size
- Peak diode current increases with C

Bridge Rectifier Circuit

ECEN 222

Maxx Seminario

Bridge Configuration:

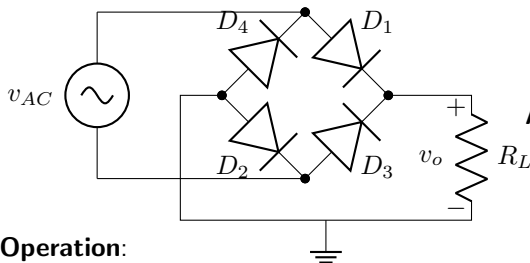

Operation:

- Positive half-cycle: D_1 , D_2 conduct
- Negative half-cycle: D_3 , D_4 conduct
- Both half-cycles produce output
- Two diodes always in series

Output Characteristics:

- v_o is always positive
- Output is full-wave rectified
- Continuous current through load

Advantages:

- 😊 No center-tap transformer needed
- 😊 Full-wave rectification
- 😊 Higher DC output
- 😊 Lower ripple frequency ($2f$)

Disadvantages:

- 😞 Two diode drops ($\approx 1.4 \text{ V}$)
- 😞 Requires four diodes

Bridge Rectifier Analysis

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

DC Output Voltage:

For ideal diodes ($V_D = 0$):

$$V_{DC} = \frac{2V_p}{\pi} \approx 0.637V_p$$


For real silicon diodes ($V_D \approx 0.7$ V each):

$$V_{DC} = \frac{2(V_p - 2V_D)}{\pi}$$

Comparison to Half-Wave:

- DC output is 2x higher
- Ripple frequency is 2x higher
- Better power utilization

Output Waveform:

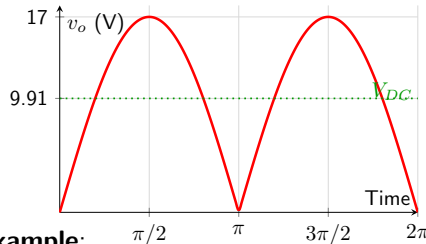

Example:

$$V_{AC,RMS} = 12 \text{ V}, V_p = 17 \text{ V}$$

$$V_{DC} = \frac{2(17 - 1.4)}{\pi} = \frac{31.14}{\pi} = 9.91 \text{ V}$$

Compare to half-wave: 5.18 V (nearly 2x improvement)

Bridge Rectifier with Filter

ECEN 222

Maxx Seminario

Introduction



Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

Filtered Bridge Rectifier:

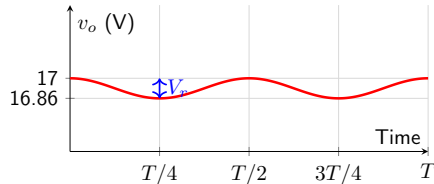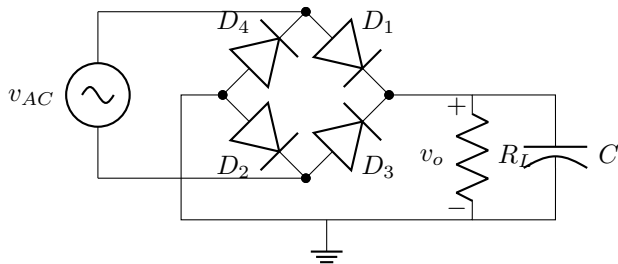

Key Difference:

Ripple frequency is $2f$

$$V_r \approx \frac{V_p}{2fR_L C}$$

Ripple is **half** that of half-wave rectifier with same C !

Design Example:

Same as before, but $f \rightarrow 2f$:

$$V_r = \frac{17}{2 \times 60 \times 2200 \times 470\mu} = 0.137 \text{ V}$$

$$V_{DC} = 17 - \frac{0.137}{2} = 16.93 \text{ V}$$

Need for Voltage Regulation

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

The Problem:

- Rectifier output varies with:
 - Input voltage changes
 - Load current changes
 - Ripple voltage
- Most circuits need stable DC
- Example: Logic circuits need $\pm 5\%$ tolerance

The Solution:

Voltage regulator:

- Maintains constant output voltage
- Compensates for input variations
- Compensates for load variations
- Types: Linear, switching, Zener

Performance Metrics:


- **Load regulation:** how much V_o changes with load
- **Line regulation:** how much V_o changes with input
- **Efficiency:** P_{out}/P_{in}

Zener Diode Shunt Regulator

ECEN 222

Maxx Seminario

Basic Shunt Regulator:

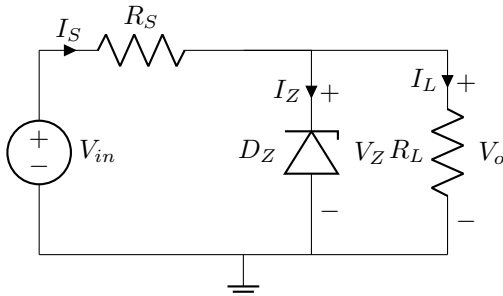

Operation Principle:

- Zener maintains constant V_Z
- R_S drops excess voltage
- Zener absorbs current variations
- $I_S = I_Z + I_L$ (KCL)

Equations of Note:

Series resistor current:

$$I_S = \frac{V_{in} - V_Z}{R_S}$$

Kirchhoff's current law:

$$I_Z = I_S - I_L$$

Zener power dissipation:

$$P_Z = V_Z \cdot I_Z$$

Design Constraints:

- $I_Z \geq I_{Z,min}$ (stay in breakdown)
- $P_Z \leq P_{Z,max}$ (power rating)
- Worst case: max I_L , min V_{in}
- Best efficiency at full load

Shunt Regulator Design Example

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

Design Specifications:

- Output: $V_o = 5.1 \text{ V}$ (use 5.1 V Zener)
- Input: $V_{in} = 12 \text{ V}$ (from rectifier)
- Load: $I_L = 0$ to 50 mA
- Zener: $I_{Z,min} = 5 \text{ mA}$, $P_{Z,max} = 0.5 \text{ W}$

Design Process:

Step 1: Find maximum safe I_Z

$$I_{Z,max} = \frac{P_{Z,max}}{V_Z} = \frac{0.5}{5.1} = 98 \text{ mA}$$

Step 2: Choose I_S for no-load condition:

At no load, $I_Z = I_S$, so choose $I_S = 90 \text{ mA}$ (safe margin below 98 mA)

Step 3: Calculate R_S

$$R_S = \frac{V_{in} - V_Z}{I_S} = \frac{12 - 5.1}{0.09} = 76.7 \Omega$$

Step 4: Verify operation at both extremes
At no load ($I_L = 0$):

$$I_Z = I_S = 90 \text{ mA}$$

$$P_Z = 5.1 \times 0.09 = 459 \text{ mW}$$

At full load ($I_L = 50 \text{ mA}$):

$$I_Z = 90 - 50 = 40 \text{ mA}$$

$$> I_{Z,min} = 5 \text{ mA}$$

Regulation Performance

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

Load Regulation:

Measures output voltage change with load current:

$$\text{Load Reg} = \frac{V_{o,no-load} - V_{o,full-load}}{V_{o,full-load}} \times 100\%$$

Affected by:

- Zener dynamic resistance r_z
- Series resistance R_S
- Load current range

Line Regulation:

Measures output voltage change with input voltage:

$$\text{Line Reg} = \frac{\Delta V_o}{\Delta V_{in}} \times 100\%$$

Efficiency:

$$\eta = \frac{P_o}{P_{in}} = \frac{V_o I_L}{V_{in} I_S} \times 100\%$$

Key Points:

- ☹ Shunt regulators have poor efficiency
- ☹ Power wasted in R_S and Zener
- 😊 Simple and inexpensive
- 😊 Good for low-power applications

Summary: Diode Applications

ECEN 222

Maxx Seminario

Introduction

Half-Wave
Rectifiers

Full-Wave
Rectifiers

Voltage
Regulation

Summary

Rectifier Circuits:

Half-Wave:

- $V_{DC} = V_p/\pi \approx 0.318V_p$
- Ripple frequency = f
- Low efficiency

Bridge (Full-Wave):

- $V_{DC} = 2V_p/\pi \approx 0.637V_p$
- Ripple frequency = $2f$
- Better efficiency

Filtering:

- Capacitor smooths output
- $V_r \approx V_p/(fR_LC)$
- Larger C reduces ripple

Voltage Regulation:

Zener Shunt Regulator:

- Maintains constant output
- $I_S = I_Z + I_L$
- $R_S = (V_{in} - V_Z)/I_S$
- Check power dissipation

Performance:

- Load regulation: ΔV_o with ΔI_L
- Line regulation: ΔV_o with ΔV_{in}
- Efficiency: typically 20-50%