

# MOSFET Applications and Frequency Response

## Unit 5: Field-Effect Transistors

Maxx Seminario

University of Nebraska-Lincoln

Spring 2026

# Lecture Overview

## Review from Last Lecture


- MOSFET small-signal models
- Transconductance ( $g_m$ )
- Output resistance ( $r_o$ )
- AC analysis techniques

## Learning Objectives

- Understand CMOS inverter operation
- Use inverter as CS amplifier
- Analyze voltage transfer characteristics
- Study MOSFET parasitic capacitances
- Determine frequency response

# The CMOS Inverter

## Circuit Configuration

 

## Operating States

$V_{in}$	NMOS	PMOS	$V_{out}$
Low (0V)	OFF	ON	High ( $V_{DD}$ )
High ( $V_{DD}$ )	ON	OFF	Low (0V)
Mid ( $V_{DD}/2$ )	ON	ON	Transition

## Key Features:


- 😊 Digital logic: inverts input signal
- 😊 Low static power consumption
- 😊 Rail-to-rail output swing

## Why CMOS?

Complementary MOS (CMOS) technology is the dominant logic family because only one transistor conducts in steady state, minimizing power dissipation.

# Voltage Transfer Characteristic (VTC)

**VTC Plot:  $V_{out}$  vs  $V_{in}$**

 

## Operating Regions

### 1. Region I: $V_{in} < V_{th,n}$

- NMOS: cutoff
- PMOS: triode
- $V_{out} = V_{DD}$

### 2. Region II: $V_{th,n} < V_{in} < V_{DD} - |V_{th,p}|$

- Both transistors in saturation
- High gain region (steep slope)

### 3. Region III: $V_{in} > V_{DD} - |V_{th,p}|$

- NMOS: triode
- PMOS: cutoff
- $V_{out} = 0$

# CMOS Inverter as Common Source Amplifier

## Biasing at Transition Point

### DC Operating Point:


- Set  $V_{in,DC} = V_{DD}/2$
- Both transistors in saturation
- $V_{out,DC} \approx V_{DD}/2$
- Maximum small-signal gain

### Voltage Gain:

$$A_v = \frac{v_{out}}{v_{in}} = \left. \frac{dV_{out}}{dV_{in}} \right|_Q < 0$$


Small input signal produces larger (inverted) output signal

## Small-Signal Operation on VTC

 

# MOSFET Internal Capacitances

## Parasitic Capacitances

 

## 1. MOSFET Capacitances


- $C_{gs}$ : gate-to-source
- $C_{gd}$ : gate-to-drain (feedback path)
- $C_{gb}$ : gate-to-body
- $C_{db}$ : drain-to-body
- $C_{sb}$ : source-to-body

### Key Points:

- In saturation:  $C_{gs}$  dominates,  $C_{gd}$  and  $C_{gb}$  are small
- $C_{gd}$  creates feedback between input and output
- Junction capacitances ( $C_{db}$ ,  $C_{sb}$ ) add to load

# Miller Effect and $C_{gd}$

## The Problem with $C_{gd}$

 


$$i_{gd} = C_{gd} \frac{d(v_{in} - v_{out})}{dt}$$

$$i_{gd} = C_{gd}(1 - A_v) \frac{dv_{in}}{dt}$$

**Miller capacitance:**

$$C_{Miller} = C_{gd}(1 - A_v) = C_{gd}(1 + |A_v|)$$

## Miller Effect Illustration

 

**Impact on Bandwidth:**



$$C_{in} = C_{gs} + C_{gd}(1 + |A_v|)$$

$$f_{3dB} = \frac{1}{2\pi R_s C_{in}}$$

where  $R_s$  is the source resistance.

# Frequency Response of Common Source Amplifier

## Complete High-Frequency Model

  

## Pole Locations:

$$\omega_{p1} = \frac{1}{R_s [C_{gs} + C_{gd}(1 + g_m R_L)]}$$

$$\omega_{p2} = \frac{1}{(r_o \parallel R_L)(C_{gd} + C_L)}$$

Usually  $\omega_{p1} < \omega_{p2}$ , so input pole dominates.

## Design Trade-offs:

- Larger  $g_m \Rightarrow$  higher gain, lower bandwidth
- Smaller  $R_s \Rightarrow$  higher bandwidth
- Smaller  $W/L \Rightarrow$  lower  $C_{gs}$ , higher bandwidth
- Load capacitance  $C_L$  limits bandwidth



# Summary and Design Considerations

## Key Concepts Covered

### 1 Common Source Amplifier

- Small-signal model:  
 $A_v = -g_m(r_o \parallel R_D)$
- Voltage gain proportional to  $g_m$
- Inverted output signal

### 2 Frequency Limitations

- Internal capacitances ( $C_{gs}$ ,  $C_{gd}$ )
- Miller effect multiplication
- Gain-bandwidth tradeoff

### 3 Practical Applications:

- Analog amplifiers
- Digital logic gates
- Mixed-signal circuits
- RF amplifiers (with special techniques)

## Design Guidelines

### For High Gain:

- 😊 Large  $g_m$  (large  $W/L$ , high  $I_D$ )
- 😊 High  $r_o$  (long channel length)
- 😞 Lower bandwidth (trade-off)

### For High Bandwidth:

- 😊 Small  $C_{gs}$  (small  $W/L$ )
- 😊 Minimize  $C_{gd}$  (small  $L_{ov}$ )
- 😊 Low source impedance
- 😞 Lower gain (trade-off)

# Practice Problem 1: CS Amplifier Gain

## Problem:

A common source amplifier has the following parameters:

- $g_m = 4 \text{ mA/V}$
- $r_o = 25 \text{ k}\Omega$
- $R_D = 2 \text{ k}\Omega$

Calculate the small-signal voltage gain.

## Solution:

Using the CS amplifier gain formula:

$$A_v = -g_m(r_o \parallel R_D) = -g_m \frac{r_o R_D}{r_o + R_D}$$

Substituting the values:

$$A_v = -4 \text{ mA/V} \times \frac{25 \text{ k}\Omega \times 2 \text{ k}\Omega}{25 \text{ k}\Omega + 2 \text{ k}\Omega} = -4 \text{ mA/V} \times 1.85 \text{ k}\Omega = -7.4 \text{ V/V}$$

**Answer:**  $A_v = -7.4 \text{ V/V}$

## Practice Problem 2: Miller Capacitance

### Problem:

For the amplifier in Problem 1, if  $C_{gd} = 15$  fF, calculate the Miller capacitance at the input.

### Given from Problem 1:

- $A_v = -7.4$  V/V
- $C_{gd} = 15$  fF

### Solution:

The Miller capacitance is given by:

$$C_{Miller} = C_{gd}(1 - A_v) = C_{gd}(1 + |A_v|)$$

Substituting the values:

$$C_{Miller} = 15 \text{ fF} \times (1 + 7.4) = 15 \text{ fF} \times 8.4 = 126 \text{ fF}$$

**Answer:**  $C_{Miller} = 126$  fF

**Note:** The feedback capacitance is multiplied by  $(1 + |A_v|)$ , increasing it by over  $8\times$ . This dramatically reduces the bandwidth.