

# Assignment 02

## Frequency Domain Analysis of Circuits

ECEN 222, Spring 2026

University of Nebraska-Lincoln

### Instructions

This assignment focuses on analyzing AC circuits in the frequency domain using phasor techniques. You will convert time-domain signals to phasors, calculate impedances, analyze circuits, and convert results back to the time domain.

### Key Formulas

#### Phasor Conversion:

$$v(t) = V_m \cos(\omega t + \phi) \quad \Leftrightarrow \quad \mathbf{V} = V_m \angle \phi$$

#### Impedances:

- Resistor:  $\mathbf{Z}_R = R$
- Inductor:  $\mathbf{Z}_L = j\omega L = \omega L \angle 90^\circ$
- Capacitor:  $\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} \angle -90^\circ$

#### Complex Number Operations:

- Rectangular to Polar:  $a + jb = \sqrt{a^2 + b^2} \angle \tan^{-1}(b/a)$
- Polar to Rectangular:  $r \angle \theta = r \cos \theta + jr \sin \theta$

#### AC Power:

- Real Power:  $P = V_{rms} I_{rms} \cos \theta$  (W)
- Reactive Power:  $Q = V_{rms} I_{rms} \sin \theta$  (VAR)
- Apparent Power:  $S = V_{rms} I_{rms}$  (VA)
- Complex Power:  $\mathbf{S} = P + jQ = \mathbf{V}_{rms} \mathbf{I}_{rms}^*$

## Problems

### 1. [12.5 points]

Given the following time-domain signals:

$$v_1(t) = 15 \cos(5000t + 60^\circ) \text{ V}$$

$$v_2(t) = 8 \cos(5000t - 30^\circ) \text{ V}$$

$$i(t) = 3 \cos(5000t + 15^\circ) \text{ A}$$

(a) Convert each signal to phasor form.

**Solution:**

For a sinusoidal signal  $v(t) = V_m \cos(\omega t + \phi)$ , the phasor is  $\mathbf{V} = V_m \angle \phi$ .

$$v_1(t) = 15 \cos(5000t + 60^\circ) \text{ V} \Rightarrow \mathbf{V}_1 = 15 \angle 60^\circ \text{ V}$$

$$v_2(t) = 8 \cos(5000t - 30^\circ) \text{ V} \Rightarrow \mathbf{V}_2 = 8 \angle -30^\circ \text{ V}$$

$$i(t) = 3 \cos(5000t + 15^\circ) \text{ A} \Rightarrow \mathbf{I} = 3 \angle 15^\circ \text{ A}$$

(b) Calculate  $\mathbf{V}_1 + \mathbf{V}_2$  in both rectangular and polar forms.

**Solution:**

First, convert each phasor to rectangular form:

$$\mathbf{V}_1 = 15 \angle 60^\circ = 15 \cos(60^\circ) + j15 \sin(60^\circ) = 7.5 + j12.99 \text{ V}$$

$$\mathbf{V}_2 = 8 \angle -30^\circ = 8 \cos(-30^\circ) + j8 \sin(-30^\circ) = 6.93 - j4.0 \text{ V}$$

Now add:

$$\begin{aligned} \mathbf{V}_1 + \mathbf{V}_2 &= (7.5 + j12.99) + (6.93 - j4.0) \\ &= 14.43 + j8.99 \text{ V} \end{aligned}$$

Convert to polar form:

$$|\mathbf{V}_1 + \mathbf{V}_2| = \sqrt{14.43^2 + 8.99^2} = \sqrt{208.22 + 80.82} = 17.00 \text{ V}$$

$$\angle(\mathbf{V}_1 + \mathbf{V}_2) = \tan^{-1} \left( \frac{8.99}{14.43} \right) = 31.9^\circ$$

**Answer:**  $\mathbf{V}_1 + \mathbf{V}_2 = 14.43 + j8.99 \text{ V} = 17.00 \angle 31.9^\circ \text{ V}$

(c) Calculate  $\mathbf{V}_1 - \mathbf{V}_2$  in both rectangular and polar forms.

**Solution:**

Using the rectangular forms from part (b):

$$\begin{aligned}\mathbf{V}_1 - \mathbf{V}_2 &= (7.5 + j12.99) - (6.93 - j4.0) \\ &= 0.57 + j16.99 \text{ V}\end{aligned}$$

Convert to polar form:

$$\begin{aligned}|\mathbf{V}_1 - \mathbf{V}_2| &= \sqrt{0.57^2 + 16.99^2} = \sqrt{0.32 + 288.66} = 17.00 \text{ V} \\ \angle(\mathbf{V}_1 - \mathbf{V}_2) &= \tan^{-1}\left(\frac{16.99}{0.57}\right) = 88.1^\circ\end{aligned}$$

**Answer:**  $\mathbf{V}_1 - \mathbf{V}_2 = 0.57 + j16.99 \text{ V} = 17.00\angle 88.1^\circ \text{ V}$

(d) Calculate the impedance  $\mathbf{Z} = \mathbf{V}_1/\mathbf{I}$  and express it in both rectangular and polar forms. What type of element(s) does this impedance represent?

**Solution:**

$$\mathbf{Z} = \frac{\mathbf{V}_1}{\mathbf{I}} = \frac{15\angle 60^\circ}{3\angle 15^\circ} = \frac{15}{3}\angle(60^\circ - 15^\circ) = 5\angle 45^\circ \Omega$$

Convert to rectangular form:


$$\mathbf{Z} = 5 \cos(45^\circ) + j5 \sin(45^\circ) = 3.54 + j3.54 \Omega$$

**Answer:**  $\mathbf{Z} = 3.54 + j3.54 \Omega = 5\angle 45^\circ \Omega$

This impedance has both a positive real part (resistive) and a positive imaginary part (inductive). It represents a resistor in series with an inductor. Since  $\omega = 5000 \text{ rad/s}$  and  $X_L = 3.54 \Omega$ , we have  $L = X_L/\omega = 3.54/5000 = 0.708 \text{ mH}$ .
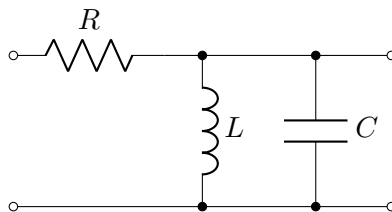
## 2. [12.5 points]

Consider a circuit with a resistor  $R = 50\ \Omega$  in series with a parallel combination of  $L = 20\text{ mH}$  and  $C = 2\ \mu\text{F}$ .



(a) Calculate the impedance of the parallel LC combination at  $f = 1000\text{ Hz}$ . Express in both rectangular and polar forms.

**Solution:**

First, calculate the angular frequency:  $\omega = 2\pi f = 2\pi(1000) = 6283.2\text{ rad/s}$

Calculate individual impedances:

$$\begin{aligned} \mathbf{Z}_L &= j\omega L = j(6283.2)(0.02) = j125.66\ \Omega \\ \mathbf{Z}_C &= \frac{1}{j\omega C} = \frac{1}{j(6283.2)(2 \times 10^{-6})} = \frac{-j}{0.01257} = -j79.58\ \Omega \end{aligned}$$

For parallel combination:

$$\begin{aligned} \mathbf{Z}_{LC} &= \frac{\mathbf{Z}_L \mathbf{Z}_C}{\mathbf{Z}_L + \mathbf{Z}_C} = \frac{(j125.66)(-j79.58)}{j125.66 - j79.58} \\ &= \frac{9999.7}{j46.08} = \frac{9999.7}{46.08 \angle 90^\circ} = 217.0 \angle -90^\circ\ \Omega \\ &= -j217.0\ \Omega \end{aligned}$$

**Answer:**  $\mathbf{Z}_{LC} = -j217.0\ \Omega = 217.0 \angle -90^\circ\ \Omega$  (capacitive)

(b) Calculate the total impedance  $\mathbf{Z}_{tot}$  at  $f = 1000\text{ Hz}$ . Express your answer in both rectangular and polar forms.

**Solution:**

The total impedance is:

$$\mathbf{Z}_{tot} = R + \mathbf{Z}_{LC} = 50 - j217.0\ \Omega$$

Convert to polar form:

$$|\mathbf{Z}_{tot}| = \sqrt{50^2 + 217.0^2} = \sqrt{2500 + 47089} = 222.7 \Omega$$

$$\angle \mathbf{Z}_{tot} = \tan^{-1} \left( \frac{-217.0}{50} \right) = -77.0^\circ$$

**Answer:**  $\mathbf{Z}_{tot} = 50 - j217.0 \Omega = 222.7 \angle -77.0^\circ \Omega$

(c) At what frequency does the parallel LC combination have infinite impedance? What is the total impedance at this frequency?

**Solution:**

Parallel LC has infinite impedance at resonance when  $\mathbf{Z}_L = -\mathbf{Z}_C$ :

$$j\omega L = - \left( \frac{-j}{\omega C} \right)$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.02)(2 \times 10^{-6})}} = \frac{1}{\sqrt{4 \times 10^{-8}}} = \frac{1}{2 \times 10^{-4}} = 5000 \text{ rad/s}$$

Corresponding frequency:

$$f_0 = \frac{\omega_0}{2\pi} = \frac{5000}{2\pi} = 795.8 \text{ Hz}$$


At this frequency, the parallel LC combination has infinite impedance (acts as an open circuit), so:

$$\mathbf{Z}_{tot}(f_0) = R + \infty \approx \infty \Omega$$

**Answer:**  $f_0 = 795.8 \text{ Hz}$ ,  $\mathbf{Z}_{tot} = 50 \Omega$  (purely resistive)
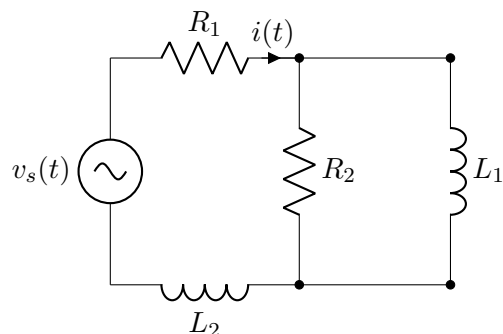
## 3. [12.5 points]

For the circuit shown below, the voltage source is  $v_s(t) = 24 \cos(3000t)$  V,  $R_1 = 30 \Omega$ ,  $R_2 = 60 \Omega$ ,  $L_1 = 20$  mH, and  $L_2 = 40$  mH.



(a) Calculate the impedances of  $L_1$  and  $L_2$  at  $\omega = 3000$  rad/s.

**Solution:**

$$\mathbf{Z}_{L_1} = j\omega L_1 = j(3000)(0.02) = j60 \Omega$$

$$\mathbf{Z}_{L_2} = j\omega L_2 = j(3000)(0.04) = j120 \Omega$$

(b) Calculate the impedance of the parallel combination of  $R_2$  and  $L_1$ .

**Solution:**

$$\begin{aligned} \mathbf{Z}_{par} &= \frac{R_2 \cdot \mathbf{Z}_{L_1}}{R_2 + \mathbf{Z}_{L_1}} = \frac{(60)(j60)}{60 + j60} = \frac{j3600}{60 + j60} \\ &= \frac{j3600}{84.85 \angle 45^\circ} = \frac{3600 \angle 90^\circ}{84.85 \angle 45^\circ} = 42.43 \angle 45^\circ \Omega \\ &= 42.43 \cos(45^\circ) + j42.43 \sin(45^\circ) = 30.0 + j30.0 \Omega \end{aligned}$$

(c) Calculate the total impedance  $\mathbf{Z}_{tot}$  in both rectangular and polar forms. (Hint: The circuit topology is  $R_1$  in series with  $(R_2 \parallel L_1)$ , all in series with  $L_2$ .)

**Solution:**

$$\begin{aligned}\mathbf{Z}_{tot} &= R_1 + \mathbf{Z}_{par} + \mathbf{Z}_{L_2} \\ &= 30 + (30.0 + j30.0) + j120 \\ &= 60.0 + j150.0 \Omega\end{aligned}$$

Convert to polar form:

$$\begin{aligned}|\mathbf{Z}_{tot}| &= \sqrt{60.0^2 + 150.0^2} = \sqrt{3600 + 22500} = 161.6 \Omega \\ \angle \mathbf{Z}_{tot} &= \tan^{-1} \left( \frac{150.0}{60.0} \right) = 68.2^\circ\end{aligned}$$

**Answer:**  $\mathbf{Z}_{tot} = 60.0 + j150.0 \Omega = 161.6 \angle 68.2^\circ \Omega$

(d) Find the current  $i(t)$  in both phasor and time-domain forms.

**Solution:**

First convert the source to phasor form:  $\mathbf{V}_s = 24 \angle 0^\circ \text{ V}$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}_{tot}} = \frac{24 \angle 0^\circ}{161.6 \angle 68.2^\circ} = 0.149 \angle -68.2^\circ \text{ A}$$

Convert to time domain:

$$i(t) = 0.149 \cos(3000t - 68.2^\circ) \text{ A} = 149 \cos(3000t - 68.2^\circ) \text{ mA}$$

**Answer:**  $\mathbf{I} = 0.149 \angle -68.2^\circ \text{ A}$ ,  $i(t) = 0.149 \cos(3000t - 68.2^\circ) \text{ A}$

(e) Find the voltage across the parallel branch and determine the current through  $R_2$  and  $L_1$  individually.

**Solution:**

Voltage across parallel branch:

$$\begin{aligned}\mathbf{V}_{par} &= \mathbf{I} \cdot \mathbf{Z}_{par} = (0.149 \angle -68.2^\circ)(42.43 \angle 45^\circ) \\ &= 6.32 \angle -23.2^\circ \text{ V}\end{aligned}$$

Current through  $R_2$ :

$$\mathbf{I}_{R_2} = \frac{\mathbf{V}_{par}}{R_2} = \frac{6.32\angle -23.2^\circ}{60} = 0.105\angle -23.2^\circ \text{ A}$$
$$i_{R_2}(t) = 0.105 \cos(3000t - 23.2^\circ) \text{ A}$$


Current through  $L_1$ :

$$\mathbf{I}_{L_1} = \frac{\mathbf{V}_{par}}{\mathbf{Z}_{L_1}} = \frac{6.32\angle -23.2^\circ}{60\angle 90^\circ} = 0.105\angle -113.2^\circ \text{ A}$$
$$i_{L_1}(t) = 0.105 \cos(3000t - 113.2^\circ) \text{ A}$$


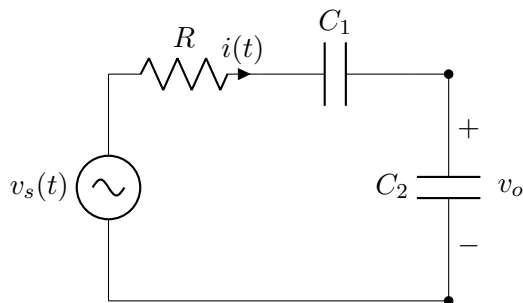
## 4. [12.5 points]

For the circuit shown below, the voltage source is  $v_s(t) = 50 \cos(4000t)$  V,  $R = 100 \Omega$ ,  $C_1 = 5 \mu\text{F}$ , and  $C_2 = 10 \mu\text{F}$ .



(a) Calculate the impedance of  $C_1$  and  $C_2$  individually at  $\omega = 4000$  rad/s.

**Solution:**

$$\begin{aligned}\mathbf{Z}_{C_1} &= \frac{1}{j\omega C_1} = \frac{1}{j(4000)(5 \times 10^{-6})} = \frac{-j}{0.02} = -j50 \Omega \\ \mathbf{Z}_{C_2} &= \frac{1}{j\omega C_2} = \frac{1}{j(4000)(10 \times 10^{-6})} = \frac{-j}{0.04} = -j25 \Omega\end{aligned}$$

(b) Calculate the total impedance  $\mathbf{Z}_{tot}$  of the three series components.

**Solution:**

$$\begin{aligned}\mathbf{Z}_{tot} &= R + \mathbf{Z}_{C_1} + \mathbf{Z}_{C_2} \\ &= 100 - j50 - j25 \\ &= 100 - j75 \Omega\end{aligned}$$

Convert to polar form:

$$\begin{aligned}|\mathbf{Z}_{tot}| &= \sqrt{100^2 + 75^2} = \sqrt{10000 + 5625} = 125 \Omega \\ \angle \mathbf{Z}_{tot} &= \tan^{-1} \left( \frac{-75}{100} \right) = -36.9^\circ\end{aligned}$$

**Answer:**  $\mathbf{Z}_{tot} = 100 - j75 \Omega = 125 \angle -36.9^\circ \Omega$

(c) Find the current  $i(t)$  in both phasor and time-domain forms.

**Solution:**

Source phasor:  $\mathbf{V}_s = 50\angle 0^\circ \text{ V}$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}_{tot}} = \frac{50\angle 0^\circ}{125\angle -36.9^\circ} = 0.4\angle 36.9^\circ \text{ A}$$

Time domain:

$$i(t) = 0.4 \cos(4000t + 36.9^\circ) \text{ A}$$

**Answer:**  $\mathbf{I} = 0.4\angle 36.9^\circ \text{ A}$ ,  $i(t) = 0.4 \cos(4000t + 36.9^\circ) \text{ A}$

(d) Find  $v_o(t)$ .

**Solution:**

The output voltage is across  $C_2$ :

$$\begin{aligned}\mathbf{V}_o &= \mathbf{I} \cdot \mathbf{Z}_{C_2} = (0.4\angle 36.9^\circ)(-j25) \\ &= (0.4\angle 36.9^\circ)(25\angle -90^\circ) \\ &= 10\angle -53.1^\circ \text{ V}\end{aligned}$$


Time domain:

$$v_o(t) = 10 \cos(4000t - 53.1^\circ) \text{ V}$$

**Answer:**  $v_o(t) = 10 \cos(4000t - 53.1^\circ) \text{ V}$
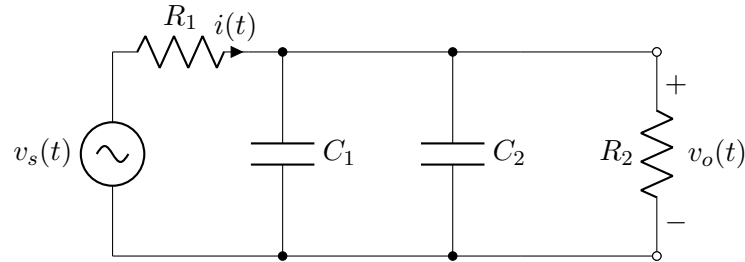
## 5. [12.5 points]

Consider the circuit shown below with  $v_s(t) = 20 \cos(8000t)$  V,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 3 \text{ k}\Omega$ ,  $C_1 = 100 \text{ nF}$ , and  $C_2 = 50 \text{ nF}$ .



(a) Calculate the impedances of  $C_1$ ,  $C_2$ , and  $R_2$  at  $\omega = 8000 \text{ rad/s}$ , then find the equivalent impedance of the parallel combination.

**Solution:**

$$\mathbf{Z}_{C_1} = \frac{1}{j\omega C_1} = \frac{1}{j(8000)(100 \times 10^{-9})} = \frac{-j}{8 \times 10^{-4}} = -j1250 \Omega$$

$$\mathbf{Z}_{C_2} = \frac{1}{j\omega C_2} = \frac{1}{j(8000)(50 \times 10^{-9})} = \frac{-j}{4 \times 10^{-4}} = -j2500 \Omega$$

$$\mathbf{Z}_{R_2} = R_2 = 3000 \Omega$$

For parallel combination:

$$\begin{aligned} \frac{1}{\mathbf{Z}_{par}} &= \frac{1}{\mathbf{Z}_{C_1}} + \frac{1}{\mathbf{Z}_{C_2}} + \frac{1}{R_2} \\ &= \frac{1}{-j1250} + \frac{1}{-j2500} + \frac{1}{3000} \\ &= j8 \times 10^{-4} + j4 \times 10^{-4} + 3.33 \times 10^{-4} \\ &= 3.33 \times 10^{-4} + j12 \times 10^{-4} \\ \mathbf{Z}_{par} &= \frac{1}{3.33 \times 10^{-4} + j12 \times 10^{-4}} = \frac{1}{12.45 \times 10^{-4} \angle 74.5^\circ} \\ &= 803.2 \angle -74.5^\circ \Omega = 214.7 - j773.8 \Omega \end{aligned}$$

**Answer:**  $\mathbf{Z}_{par} = 214.7 - j773.8 \Omega = 803.2 \angle -74.5^\circ \Omega$

(b) Calculate the total circuit impedance  $\mathbf{Z}_{tot}$  in both rectangular and polar forms.

**Solution:**

$$\begin{aligned}\mathbf{Z}_{tot} &= R_1 + \mathbf{Z}_{par} = 1000 + (214.7 - j773.8) \\ &= 1214.7 - j773.8 \Omega\end{aligned}$$

Polar form:

$$\begin{aligned}|\mathbf{Z}_{tot}| &= \sqrt{1214.7^2 + 773.8^2} = \sqrt{1475496 + 598766} = 1441 \Omega \\ \angle \mathbf{Z}_{tot} &= \tan^{-1} \left( \frac{-773.8}{1214.7} \right) = -32.5^\circ\end{aligned}$$

**Answer:**  $\mathbf{Z}_{tot} = 1214.7 - j773.8 \Omega = 1441 \angle -32.5^\circ \Omega$

(c) Find the input current  $i(t)$  in both phasor and time-domain forms.

**Solution:**

Source phasor:  $\mathbf{V}_s = 20 \angle 0^\circ \text{ V}$

$$\mathbf{I} = \frac{\mathbf{V}_s}{\mathbf{Z}_{tot}} = \frac{20 \angle 0^\circ}{1441 \angle -32.5^\circ} = 0.01388 \angle 32.5^\circ \text{ A}$$

Time domain:

$$i(t) = 0.01388 \cos(8000t + 32.5^\circ) \text{ A} = 13.88 \cos(8000t + 32.5^\circ) \text{ mA}$$

**Answer:**  $\mathbf{I} = 13.88 \angle 32.5^\circ \text{ mA}$ ,  $i(t) = 13.88 \cos(8000t + 32.5^\circ) \text{ mA}$

(d) Find the output voltage  $v_o(t)$ .

**Solution:**

Output voltage across parallel combination:

$$\begin{aligned}\mathbf{V}_o &= \mathbf{I} \cdot \mathbf{Z}_{par} = (0.01388 \angle 32.5^\circ)(803.2 \angle -74.5^\circ) \\ &= 11.15 \angle -42.0^\circ \text{ V}\end{aligned}$$

Time domain:

$$v_o(t) = 11.15 \cos(8000t - 42.0^\circ) \text{ V}$$

**Answer:**  $v_o(t) = 11.15 \cos(8000t - 42.0^\circ) \text{ V}$

(e) Calculate the magnitude ratio  $|\mathbf{V}_o|/|\mathbf{V}_s|$  and the phase shift.

**Solution:**

$$\text{Magnitude ratio: } \frac{|\mathbf{V}_o|}{|\mathbf{V}_s|} = \frac{11.15}{20} = 0.5575$$

$$\text{Phase shift: } \Delta\phi = -42.0^\circ - 0^\circ = -42.0^\circ$$

This circuit acts as a voltage divider with gain of 0.56 and introduces a phase lag of  $42.0^\circ$ .

**Answer:** Magnitude ratio = 0.5575, Phase shift =  $-42.0^\circ$

(f) Find the current through each capacitor ( $C_1$  and  $C_2$ ) individually.

**Solution:**

Current through  $C_1$ :

$$\begin{aligned} \mathbf{I}_{C_1} &= \frac{\mathbf{V}_o}{\mathbf{Z}_{C_1}} = \frac{11.15\angle -42.0^\circ}{-j1250} = \frac{11.15\angle -42.0^\circ}{1250\angle -90^\circ} \\ &= 0.00892\angle 48.0^\circ \text{ A} = 8.92\angle 48.0^\circ \text{ mA} \\ i_{C_1}(t) &= 8.92 \cos(8000t + 48.0^\circ) \text{ mA} \end{aligned}$$

Current through  $C_2$ :

$$\begin{aligned} \mathbf{I}_{C_2} &= \frac{\mathbf{V}_o}{\mathbf{Z}_{C_2}} = \frac{11.15\angle -42.0^\circ}{-j2500} = \frac{11.15\angle -42.0^\circ}{2500\angle -90^\circ} \\ &= 0.00446\angle 48.0^\circ \text{ A} = 4.46\angle 48.0^\circ \text{ mA} \\ i_{C_2}(t) &= 4.46 \cos(8000t + 48.0^\circ) \text{ mA} \end{aligned}$$

## 6. [12.5 points]

A load is connected to an AC source. The voltage across the load and the current through the load are measured as:

$$\begin{aligned}v(t) &= 120\sqrt{2}\cos(377t) \text{ V} \\i(t) &= 6\sqrt{2}\cos(377t - 53.13^\circ) \text{ A}\end{aligned}$$

(a) Convert the voltage and current to phasor form, then calculate the RMS phasors  $\mathbf{V}_{rms}$  and  $\mathbf{I}_{rms}$ . (Hint: The  $\sqrt{2}$  factor is included to indicate peak values.)

**Solution:**

The signals are already in peak form. Convert to phasors:

$$\begin{aligned}v(t) &= 120\sqrt{2}\cos(377t) \text{ V} \Rightarrow \mathbf{V} = 120\sqrt{2}\angle 0^\circ \text{ V} \\i(t) &= 6\sqrt{2}\cos(377t - 53.13^\circ) \text{ A} \Rightarrow \mathbf{I} = 6\sqrt{2}\angle -53.13^\circ \text{ A}\end{aligned}$$

RMS values:

$$\begin{aligned}\mathbf{V}_{rms} &= \frac{\mathbf{V}}{\sqrt{2}} = \frac{120\sqrt{2}}{\sqrt{2}}\angle 0^\circ = 120\angle 0^\circ \text{ V} \\ \mathbf{I}_{rms} &= \frac{\mathbf{I}}{\sqrt{2}} = \frac{6\sqrt{2}}{\sqrt{2}}\angle -53.13^\circ = 6\angle -53.13^\circ \text{ A}\end{aligned}$$

**Answer:**  $\mathbf{V}_{rms} = 120\angle 0^\circ \text{ V}$ ,  $\mathbf{I}_{rms} = 6\angle -53.13^\circ \text{ A}$

(b) Find the real power  $P$ , reactive power  $Q$ , and apparent power  $\mathbf{S}$ . Include proper units.

**Solution:**

The phase angle between voltage and current is  $\theta = 0^\circ - (-53.13^\circ) = 53.13^\circ$ .

$$\begin{aligned}S &= V_{rms}I_{rms} = (120)(6) = 720 \text{ VA} \\P &= V_{rms}I_{rms}\cos\theta = (120)(6)\cos(53.13^\circ) = 720(0.6) = 432 \text{ W} \\Q &= V_{rms}I_{rms}\sin\theta = (120)(6)\sin(53.13^\circ) = 720(0.8) = 576 \text{ VAR}\end{aligned}$$

Alternatively, using complex power:

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{rms}\mathbf{I}_{rms}^* = (120\angle 0^\circ)(6\angle 53.13^\circ) \\&= 720\angle 53.13^\circ = 432 + j576 \text{ VA}\end{aligned}$$

**Answer:**  $P = 432 \text{ W}$ ,  $Q = 576 \text{ VAR}$  (inductive),  $S = 720 \text{ VA}$ ,  $\mathbf{S} = 432 + j576 \text{ VA}$

(c) Calculate the power factor and state whether the load is inductive or capacitive. Explain your reasoning.

**Solution:**

$$\text{Power factor} = \cos \theta = \cos(53.13^\circ) = 0.6 \text{ lagging}$$

The load is **inductive** because:

- The current lags the voltage by  $53.13^\circ$  (current phase angle is  $-53.13^\circ$  while voltage is at  $0^\circ$ )
- Reactive power  $Q > 0$  (positive reactive power indicates inductive load)
- The power factor is "lagging"

**Answer:** Power factor = 0.6 lagging, Load is inductive

(d) Find the impedance of the load using  $\mathbf{Z} = \mathbf{V}_{rms}/\mathbf{I}_{rms}$  in both rectangular and polar forms. What circuit elements could this load represent?

**Solution:**

$$\mathbf{Z} = \frac{\mathbf{V}_{rms}}{\mathbf{I}_{rms}} = \frac{120\angle 0^\circ}{6\angle -53.13^\circ} = 20\angle 53.13^\circ \Omega$$

Convert to rectangular form:

$$\begin{aligned}\mathbf{Z} &= 20 \cos(53.13^\circ) + j20 \sin(53.13^\circ) \\ &= 20(0.6) + j20(0.8) = 12 + j16 \Omega\end{aligned}$$

This impedance represents a resistor in series with an inductor:

$$\begin{aligned}R &= 12 \Omega \\ X_L = 16 \Omega &\Rightarrow L = \frac{X_L}{\omega} = \frac{16}{377} = 42.4 \text{ mH}\end{aligned}$$

**Answer:**  $\mathbf{Z} = 12 + j16 \Omega = 20\angle 53.13^\circ \Omega$ . The load is a  $12 \Omega$  resistor in series with a  $42.4 \text{ mH}$  inductor.

(e) If you wanted to improve the power factor to unity (1.0), what value of capacitor would you need to place in parallel with this load? (Note:  $\omega = 377 \text{ rad/s}$  corresponds to  $f = 60 \text{ Hz}$ )

**Solution:**

To achieve unity power factor, we need to cancel the reactive power:

$$Q_C = -Q_L = -576 \text{ VAR}$$

For a capacitor:


$$\begin{aligned} Q_C &= -V_{rms}^2 \omega C \quad (\text{negative because capacitive}) \\ -576 &= -\frac{V_{rms}^2}{X_C} = -V_{rms}^2 \omega C \\ 576 &= (120)^2 \omega C \\ C &= \frac{576}{(120)^2(377)} = \frac{576}{5428800} = 106.1 \times 10^{-6} \text{ F} \end{aligned}$$

**Answer:**  $C = 106.1 \mu\text{F}$  (placed in parallel with the load)


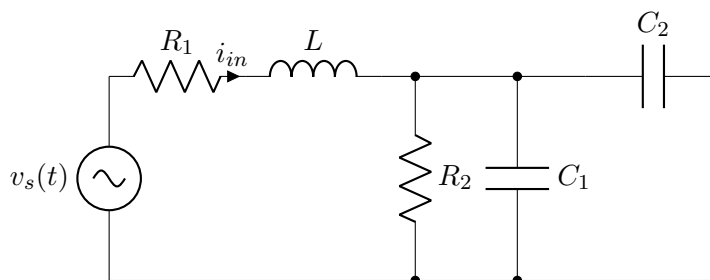
## 7. [12.5 points]

Consider the circuit with  $v_s(t) = 100 \cos(5000t)$  V,  $R_1 = 20 \Omega$ ,  $R_2 = 80 \Omega$ ,  $L = 8$  mH,  $C_1 = 10 \mu\text{F}$ , and  $C_2 = 40 \mu\text{F}$ .



(a) Calculate all component impedances at  $\omega = 5000$  rad/s.

**Solution:**

$$\mathbf{Z}_{R_1} = R_1 = 20 \Omega$$

$$\mathbf{Z}_{R_2} = R_2 = 80 \Omega$$

$$\mathbf{Z}_L = j\omega L = j(5000)(0.008) = j40 \Omega$$

$$\mathbf{Z}_{C_1} = \frac{1}{j\omega C_1} = \frac{1}{j(5000)(10 \times 10^{-6})} = \frac{-j}{0.05} = -j20 \Omega$$

$$\mathbf{Z}_{C_2} = \frac{1}{j\omega C_2} = \frac{1}{j(5000)(40 \times 10^{-6})} = \frac{-j}{0.2} = -j5 \Omega$$

(b) Calculate the total impedance  $\mathbf{Z}_{tot}$  in both rectangular and polar forms.

**Solution:**

The circuit topology is:  $R_1$  in series with  $L$ , then parallel combination of  $(R_2 \parallel C_1 \parallel C_2)$ .

First, find the parallel impedance:

$$\begin{aligned} \frac{1}{\mathbf{Z}_{par}} &= \frac{1}{R_2} + \frac{1}{\mathbf{Z}_{C_1}} + \frac{1}{\mathbf{Z}_{C_2}} \\ &= \frac{1}{80} + \frac{1}{-j20} + \frac{1}{-j5} \\ &= 0.0125 + j0.05 + j0.2 = 0.0125 + j0.25 \\ \mathbf{Z}_{par} &= \frac{1}{0.0125 + j0.25} = \frac{1}{0.2503 \angle 87.1^\circ} = 3.996 \angle -87.1^\circ \Omega \\ &= 0.20 - j3.99 \Omega \end{aligned}$$

Total impedance:

$$\begin{aligned}\mathbf{Z}_{tot} &= R_1 + \mathbf{Z}_L + \mathbf{Z}_{par} \\ &= 20 + j40 + (0.20 - j3.99) \\ &= 20.20 + j36.01 \Omega\end{aligned}$$

Polar form:

$$\begin{aligned}|\mathbf{Z}_{tot}| &= \sqrt{20.20^2 + 36.01^2} = \sqrt{408.04 + 1296.72} = 41.29 \Omega \\ \angle \mathbf{Z}_{tot} &= \tan^{-1} \left( \frac{36.01}{20.20} \right) = 60.7^\circ\end{aligned}$$

**Answer:**  $\mathbf{Z}_{tot} = 20.20 + j36.01 \Omega = 41.29 \angle 60.7^\circ \Omega$

(c) Find the input current  $i_{in}(t)$  in both phasor and time-domain forms.

**Solution:**

Source phasor:  $\mathbf{V}_s = 100 \angle 0^\circ \text{ V}$

$$\mathbf{I}_{in} = \frac{\mathbf{V}_s}{\mathbf{Z}_{tot}} = \frac{100 \angle 0^\circ}{41.29 \angle 60.7^\circ} = 2.42 \angle -60.7^\circ \text{ A}$$

Time domain:

$$i_{in}(t) = 2.42 \cos(5000t - 60.7^\circ) \text{ A}$$

**Answer:**  $\mathbf{I}_{in} = 2.42 \angle -60.7^\circ \text{ A}$ ,  $i_{in}(t) = 2.42 \cos(5000t - 60.7^\circ) \text{ A}$

(d) Calculate the voltage across the parallel branch ( $R_2 \parallel C_1 \parallel C_2$ ).

**Solution:**

$$\begin{aligned}\mathbf{V}_{par} &= \mathbf{I}_{in} \cdot \mathbf{Z}_{par} = (2.42 \angle -60.7^\circ)(3.996 \angle -87.1^\circ) \\ &= 9.67 \angle -147.8^\circ \text{ V}\end{aligned}$$

Time domain:

$$v_{par}(t) = 9.67 \cos(5000t - 147.8^\circ) \text{ V}$$

**Answer:**  $\mathbf{V}_{par} = 9.67\angle -147.8^\circ \text{ V}$

(e) Find the current through  $R_2$ ,  $C_1$ , and  $C_2$  individually.

**Solution:**

Current through  $R_2$ :

$$\begin{aligned}\mathbf{I}_{R_2} &= \frac{\mathbf{V}_{par}}{R_2} = \frac{9.67\angle -147.8^\circ}{80} = 0.121\angle -147.8^\circ \text{ A} \\ i_{R_2}(t) &= 0.121 \cos(5000t - 147.8^\circ) \text{ A} = 121 \cos(5000t - 147.8^\circ) \text{ mA}\end{aligned}$$

Current through  $C_1$ :


$$\begin{aligned}\mathbf{I}_{C_1} &= \frac{\mathbf{V}_{par}}{\mathbf{Z}_{C_1}} = \frac{9.67\angle -147.8^\circ}{-j20} = \frac{9.67\angle -147.8^\circ}{20\angle -90^\circ} \\ &= 0.484\angle -57.8^\circ \text{ A} \\ i_{C_1}(t) &= 0.484 \cos(5000t - 57.8^\circ) \text{ A} = 484 \cos(5000t - 57.8^\circ) \text{ mA}\end{aligned}$$

Current through  $C_2$ :

$$\begin{aligned}\mathbf{I}_{C_2} &= \frac{\mathbf{V}_{par}}{\mathbf{Z}_{C_2}} = \frac{9.67\angle -147.8^\circ}{-j5} = \frac{9.67\angle -147.8^\circ}{5\angle -90^\circ} \\ &= 1.934\angle -57.8^\circ \text{ A} \\ i_{C_2}(t) &= 1.934 \cos(5000t - 57.8^\circ) \text{ A}\end{aligned}$$
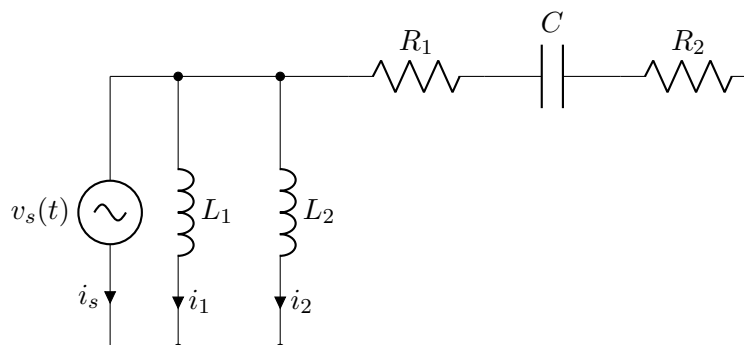
## 8. [12.5 points]

Analyze the circuit shown below with  $v_s(t) = 60 \cos(4000t)$  V,  $R_1 = 50 \Omega$ ,  $R_2 = 100 \Omega$ ,  $L_1 = 25$  mH,  $L_2 = 50$  mH, and  $C = 5 \mu\text{F}$ .



(a) Calculate the impedance of each inductor and the capacitor at  $\omega = 4000$  rad/s.

**Solution:**

$$\mathbf{Z}_{L_1} = j\omega L_1 = j(4000)(0.025) = j100 \Omega$$

$$\mathbf{Z}_{L_2} = j\omega L_2 = j(4000)(0.050) = j200 \Omega$$

$$\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{1}{j(4000)(5 \times 10^{-6})} = \frac{-j}{0.02} = -j50 \Omega$$

(b) Calculate the equivalent impedance of the parallel inductor combination ( $L_1 \parallel L_2$ ).

**Solution:**

$$\begin{aligned} \mathbf{Z}_{L,par} &= \frac{\mathbf{Z}_{L_1} \cdot \mathbf{Z}_{L_2}}{\mathbf{Z}_{L_1} + \mathbf{Z}_{L_2}} = \frac{(j100)(j200)}{j100 + j200} \\ &= \frac{-20000}{j300} = \frac{-20000}{300 \angle 90^\circ} = \frac{20000}{300} \angle -90^\circ \\ &= 66.67 \angle 90^\circ = j66.67 \Omega \end{aligned}$$

Alternatively, for inductors in parallel:

$$\begin{aligned} L_{eq} &= \frac{L_1 L_2}{L_1 + L_2} = \frac{(0.025)(0.050)}{0.025 + 0.050} = \frac{0.00125}{0.075} = 0.01667 \text{ H} \\ \mathbf{Z}_{L,par} &= j\omega L_{eq} = j(4000)(0.01667) = j66.67 \Omega \end{aligned}$$

**Answer:**  $\mathbf{Z}_{L,par} = j66.67 \Omega$

(c) Calculate the total impedance  $\mathbf{Z}_{tot}$  in both rectangular and polar forms.

**Solution:**

First, calculate the series impedance:

$$\begin{aligned}\mathbf{Z}_{series} &= R_1 + \mathbf{Z}_C + R_2 \\ &= 50 - j50 + 100 \\ &= 150 - j50 \Omega\end{aligned}$$

Now find the parallel combination:

$$\begin{aligned}\mathbf{Z}_{tot} &= \frac{\mathbf{Z}_{L,par} \cdot \mathbf{Z}_{series}}{\mathbf{Z}_{L,par} + \mathbf{Z}_{series}} = \frac{(j66.67)(150 - j50)}{j66.67 + 150 - j50} \\ &= \frac{j66.67(150 - j50)}{150 + j16.67} = \frac{j10000.5 + 3333.5}{150 + j16.67} \\ &= \frac{3333.5 + j10000.5}{150 + j16.67}\end{aligned}$$

Convert to polar:

$$\begin{aligned}\text{Numerator: } |3333.5 + j10000.5| &= \sqrt{3333.5^2 + 10000.5^2} = 10543 \Omega \\ \angle &= \tan^{-1}(10000.5/3333.5) = 71.6^\circ \\ \text{Denominator: } |150 + j16.67| &= \sqrt{150^2 + 16.67^2} = 150.9 \Omega \\ \angle &= \tan^{-1}(16.67/150) = 6.34^\circ\end{aligned}$$

$$\mathbf{Z}_{tot} = \frac{10543 \angle 71.6^\circ}{150.9 \angle 6.34^\circ} = 69.87 \angle 65.3^\circ \Omega$$

Convert to rectangular:

$$\mathbf{Z}_{tot} = 69.87 \cos(65.3^\circ) + j69.87 \sin(65.3^\circ) = 29.1 + j63.5 \Omega$$

**Answer:**  $\mathbf{Z}_{tot} = 29.1 + j63.5 \Omega = 69.87 \angle 65.3^\circ \Omega$

(d) Find the total source current  $i_s(t)$  in both phasor and time-domain forms.

**Solution:**

Source phasor:  $\mathbf{V}_s = 60\angle 0^\circ \text{ V}$

$$\mathbf{I}_s = \frac{\mathbf{V}_s}{\mathbf{Z}_{tot}} = \frac{60\angle 0^\circ}{69.87\angle 65.3^\circ} = 0.859\angle -65.3^\circ \text{ A}$$

Time domain:

$$i_s(t) = 0.859 \cos(4000t - 65.3^\circ) \text{ A} = 859 \cos(4000t - 65.3^\circ) \text{ mA}$$

**Answer:**  $\mathbf{I}_s = 0.859\angle -65.3^\circ \text{ A}$ ,  $i_s(t) = 0.859 \cos(4000t - 65.3^\circ) \text{ A}$

(e) Find the voltage across the parallel inductor combination, then determine the individual currents  $i_1(t)$  and  $i_2(t)$  through each inductor.

**Solution:**

Since the inductors are in parallel with the entire circuit and connected directly to the source, the voltage across them is the source voltage:

$$\mathbf{V}_{L,par} = \mathbf{V}_s = 60\angle 0^\circ \text{ V}$$

Current through  $L_1$ :

$$\begin{aligned} \mathbf{I}_1 &= \frac{\mathbf{V}_{L,par}}{\mathbf{Z}_{L_1}} = \frac{60\angle 0^\circ}{100\angle 90^\circ} = 0.6\angle -90^\circ \text{ A} \\ i_1(t) &= 0.6 \cos(4000t - 90^\circ) \text{ A} = 600 \cos(4000t - 90^\circ) \text{ mA} \end{aligned}$$

Current through  $L_2$ :

$$\begin{aligned} \mathbf{I}_2 &= \frac{\mathbf{V}_{L,par}}{\mathbf{Z}_{L_2}} = \frac{60\angle 0^\circ}{200\angle 90^\circ} = 0.3\angle -90^\circ \text{ A} \\ i_2(t) &= 0.3 \cos(4000t - 90^\circ) \text{ A} = 300 \cos(4000t - 90^\circ) \text{ mA} \end{aligned}$$

Current through series branch ( $R_1 + C + R_2$ ):

$$\begin{aligned} \mathbf{I}_{series} &= \frac{\mathbf{V}_s}{\mathbf{Z}_{series}} = \frac{60\angle 0^\circ}{150 - j50} = \frac{60\angle 0^\circ}{158.1\angle -18.4^\circ} \\ &= 0.379\angle 18.4^\circ \text{ A} \end{aligned}$$

Verification:  $\mathbf{I}_s = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_{series}$  (by current division)

(f) Calculate the total real power, reactive power, and complex power delivered by the source. Express complex power in rectangular form. (Hint: You already know the source voltage and current.)

**Solution:**

Convert to RMS values:

$$\mathbf{V}_{s,rms} = \frac{60}{\sqrt{2}} \angle 0^\circ = 42.43 \angle 0^\circ \text{ V}$$
$$\mathbf{I}_{s,rms} = \frac{0.859}{\sqrt{2}} \angle -65.3^\circ = 0.607 \angle -65.3^\circ \text{ A}$$

Complex power:

$$\begin{aligned}\mathbf{S} &= \mathbf{V}_{s,rms} \mathbf{I}_{s,rms}^* = (42.43 \angle 0^\circ)(0.607 \angle 65.3^\circ) \\ &= 25.76 \angle 65.3^\circ \text{ VA}\end{aligned}$$

Convert to rectangular form:

$$\begin{aligned}\mathbf{S} &= 25.76 \cos(65.3^\circ) + j25.76 \sin(65.3^\circ) \\ &= 10.74 + j23.43 \text{ VA}\end{aligned}$$

Therefore:

$$\begin{aligned}P &= 10.74 \text{ W (real power)} \\ Q &= 23.43 \text{ VAR (reactive power, inductive)} \\ S &= |\mathbf{S}| = 25.76 \text{ VA (apparent power)}\end{aligned}$$

**Answer:**  $P = 10.74 \text{ W}$ ,  $Q = 23.43 \text{ VAR}$ ,  $\mathbf{S} = 10.74 + j23.43 \text{ VA}$